
| Seat No.: Enro | llment No. |
|----------------|------------|
|----------------|------------|

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

BE – SEMESTER-III (NEW) • EXAMINATION – SUMMER-2015

| Subject Code: 2132003 Subject Name: Design Concepts in Basic Electronics Time:02.30pm-05.00pm Instructions: |            | Date:27/05/2015  Total Marks: 70  |                   |            |
|---|------------|---|-------------------|------------|
|   |            |   |                   |            |
| Q.1   | (a)<br>(b) | <ol> <li>Answer the following question.         <ol> <li>Define Digital System.</li> <li>Convert (2C6B.F2)<sub>16</sub> into its equivalent Binary.</li> <li>Convert (8)<sub>10</sub> into equivalent BCD and Excess-3 code.</li> <li>Convert (414)<sub>8</sub> into its equivalent Hexadecimal and Binar</li> </ol> </li> <li>Comparison between 1's and 2's compliments.</li> <li>Explain Digital Logic Gates with Symbol, Algebraic function an</li> </ol> |                   | 03         |
| Q.2   | (a)        | 1) State the truth table of full-adder and half-adder.  |                   | 0.         |
|   | <b>(b)</b> | 2) Draw the logic diagram and state truth table of 4x1 multiplex Draw and Explain the working of clocked RS flip-flop.  OR  | er.               | 04         |
|   | <b>(b)</b> | Draw and Explain the working of JK flip-flop.   |                   | 0'         |
| Q.3   | (a)<br>(b) | Design 4-bit up-down binary counter with the help of T flip-flop<br>Define term Register. Define the 'Different Modes of Operation<br><b>OR</b>   |                   | 0′<br>0′   |
| Q.3   | (a)<br>(b) | With the logic diagram explain the operation of 4-bit binary ripp Explain with neat diagram working of 4-bit bidirectional shaparallel load.  |                   | 0'.<br>0'. |
| Q.4   | (a)<br>(b) | Explain Forward Bias and Reverse Bias.  Give the points of difference between Half wave, Full wave and OR   | Bridge Rectifier. | 0'.<br>0'. |
| Q.4   | (a)<br>(b) | Explain in detail different types of breakdown in diode.<br>Explain different configuration of clippers.  |                   | 0'.<br>0'. |
| Q.5   | (a)        | Explain the input output characteristics of n-p-n transistor in Coconfiguration.  | ommon-Collector   | 0'         |
|   | <b>(b)</b> | Draw fixed-bias circuit and explain Collector-Emitter loop.  OR   |                   | 0'         |
| Q.5   | (a)        | Explain the input output characteristics of p-n-p transistor in configuration.  | Common-Emitter    | 0′         |

**07** 

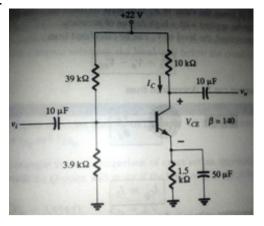

\*\*\*\*\*