Seat No.:	Enrolment No
-----------	--------------

Subject Code: 2142405

## GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER- IV(NEW) EXAMINATION - SUMMER 2015

Date:28/05/2015

Ti	me: i	. Attempt all questions.  2. Make suitable assumptions wherever necessary.	0
Q.1	<ul><li>(a)</li><li>(b)</li></ul>	Draw and Explain full wave bridge rectifier circuit with capacitor filter draw necessary waveforms. $100\mu F$ capacitor when used as a filter has 12V dc across it with a terminal load resistor of $2.5K\Omega$ . If the rectifier is full wave and supply frequency is $50Hz$ what is	07 07
Q.2	(a)	the percentage of ripple in the output.  Draw the block diagram of a regulated DC power supply and explain the function of each block.	07
	<b>(b)</b>	Draw the circuit diagram of class B push pull amplifier with the help of suitable waveforms and explain its operation.	07
	<b>(b)</b>	<b>OR</b> Draw the CE transistor configuration and give its input and output characteristics.	07
Q.3	(a)	Explain block diagram of op-amp. Explain function of each block.	07
	<b>(b)</b>	Explain the construction of ANDgate,OR gate, Not gate logic gates using discrete components like diode, resistor, Transistor etc.  OR	07
Q.3	(a)	Explain inverting and non-inverting and differential amplifier using op-amp under open loop condition	07
	<b>(b)</b>	Why NAND gate and NOR gate is known as a Universal Gate? Obtain AND gate, OR gate and Exclusive-OR gate using NAND gate and NOR gate.	07
Q.4	(a)	Explain the following terms related to the Op-amp:1)Input offset voltage 2) Input bias & offset current3) Total output offset voltage 4)PSRR 5)CMRR	07
	<b>(b)</b>	Explain Zero Crossing Detector circuit	07
		OR	
Q.4	(a) (b)	Explain the Op-amp based Precision Rectifier circuit Explain Op-amp based Clipper & Clamper circuit	07 07
Q.5	(a) (b)	Explain Switched Capacitor Filter circuit in detail Explain Suming, Scaling and Averaging Amplifier circuit	07 07
Q.5	(a)	<b>OR</b> Define the Active and Passive Filter and Explain the op-amp based High Pass Filter circuit.	07
	<b>(b)</b>	Define Oscillators enlist types of oscillators and Explain op-amp based phase Shift Oscillator in detail	07

\*\*\*\*\*