## **GUJARAT TECHNOLOGICAL UNIVERSITY** BE- IV<sup>th</sup> SEMESTER-EXAMINATION – MAY/JUNE- 2012

Subject code: 141101

**Subject Name: Advance Electronics** 

Time: 10:30 am – 01:00 pm

# **Instructions:**

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Derive CE current gain for finite value Resistive load using  $\pi$  model and 07 prove that 3-dB band width of this configuration is inversely proportional to the value of the resistive load
  - (b) Classify distortion in an amplifier and explain each, briefly 07
- Q.2 (a) Multistage amplifier consists of 3-stages and voltage gain of each stage 07 is 50, 60 and 80 respectively. Find (1) Overall gain in dB (2) if multi stage input is  $10 \,\mu$ V, what is the final output?
  - (b) Describe the principle of crystal oscillator along with its equivalent 07 circuit

### OR

- (b) What is diffusion capacitance? Derive value of diffusion capacitance in 07 terms of physical parameters of transistor
- Q.3 (a) Draw equivalent circuit of voltage & current amplifier and discuss on the 07 value of input and output impedance. Also Classify distortion in an amplifier and explain each, briefly
  - (b) CE transistor hybrid  $\pi$  model parameters are as follows:  $g_m = 50 \text{ mA/V}$ , 07  $r_{b'e} = 1K\Omega$ ,  $r_{bb'} = 10\Omega$ ,  $C_{b'e} = 101 \text{ pF}$ ,  $C_{b'c} = 3.5 \text{ pF}$ . Find (1)3-dB bandwidth for  $R_L = 1K\Omega$  (2) Gain at 1 MHz frequency

#### OR

- Q.3 (a) Discuss validity of hybrid  $\pi$  model and prove that the model is valid up 07 to one third of  $f_T$ 
  - (b) Frequency sensitive arm of Wein-bridge oscillator uses  $R_1 = R_2 = 10 \text{ k}\Omega$  07 while  $C_1 = C_2$ , is kept variable. Find Minimum and maximum value of Capacitance to achieve output frequency range from 20 KHz to 70 KHz
- Q.4 (a) Explain emitter coupled differential amplifier in brief. How its 07 performance can be improved
  - (b) Derive gain equation for Op Amp for inverting and non inverting mode 07 and derive equation for Common mode rejection Ratio (CMRR). Why CMRR should be ideally high.

### OR

- Q.4 (a) List the characteristic of Ideal Op Amp. Two set of inputs for differential 07 amplifier are (i)  $V_1 = 100 \mu V$ , (ii)  $V_2 = -100 \mu V \& V_1 = 1100 \mu V$ , (ii)  $V_2 = 900 \mu V$ . For CMRR = 200 Calculate %difference in output Voltage. If CMRR changed to 20000. Calculate %difference in output Voltage
  - (b) Discuss the effect of positive feedback and negative feed back on a **07** transistor amplifier circuit. Which feed back improves the stability? Which one creates instability & what is the application of feed back which create the instability? Explain with appropriate condition

**Total Marks: 70** 

Date: 25/05/2012

1

- Q.5 (a) Draw NOR gate circuit using RTL logic. Explain its operation and list 07 disadvantages
  - (b) Explain requirement of Digital to Analog converter and draw and 07 explain the weighted resistor type (4-bit) Digital to Analog converter.

OR

- Q.5 (a) Draw circuit of two input TTL NAND GATE. Explain its working.O7 Compare it with RTL in terms of speed and power consumption with reasoning
  - (b) Draw and explain track type analog to digital converter. In terms of **07** speed is it better than the counter type ? Give reason in support to your answer

\*\*\*\*