Seat No.: ____

Enrolment No._____

GUJARAT TECHNOLOGICAL UNIVERSITY BE- Vth SEMESTER-EXAMINATION – MAY/JUNE - 2012

BE- V^{III} SEMESTER-EXAMINATION – MAY/JUNE - 2012			
Subject code: 151006 Date: 07/06/2012			
Subject Name: Applied Electronics			
Time: 02:30 pm – 05:00 pm Total Marks: 70			
Instructions:			
		Attempt all questions. Make quitable assumptions wherever passagery	
		Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
	з.	rigures to the right indicate run marks.	
Q.1	(a)	Define following terms:	07
V .1	(4)	(i) Ideal Voltage source (ii) Ideal current source (iii) Dependent Voltage source	07
		(iv) Dependent current source (v) Load side regulation (vi) Line side regulation	
		(vii) Regulated power supply.	
	(b)		07
	(0)	Diseass any one erosed - Loop op and configurations in acam	07
Q.2	(a)	How to use 555 as monostable multivibrator?	07
	(b)		07
	. ,	OR	
	(b)	Explain the working of photoconductive sensors and photovoltaic sensors in detail.	07
Q.3	(a)	Discuss following:	07
		(i) Electrical strain gauge (ii) Thermocouple (iii) thermistor	
	(b)	For the inverting amplifier with feedback, $R1 = 500 \Omega$ and $R_F = 4.7 \text{ K}\Omega$. Assume	07
		that A = 200000, $R_i = 2 M\Omega$, Ro = 75 Ω , fo = 5Hz, Supply voltages = ± 15V,	
		Output voltage swing = \pm 13V. Calculate the values of A _F , Ri _F , Ro _F , f _F , and Voo _T .	
		OR	
Q.3	(a)		07
		(i) Input offset voltage (ii) Input offset voltage (iii) Input bias current (iv) Input	
		capacitance (v) Slew rate (vi) SVRR (vii) CMRR	
			07
	(b)	Design a square wave generator at 1KHz using 555 timer IC.	07
Q.4	(a)	Explain construction and working of SCR using two transistor model.	07
X ···	(b)		07
		OR	-
Q.4	(a)	Explain construction and working of UJT. Also explain UJT as relaxation oscillator.	07
•	(b)	· · ·	07
Q.5	(a)	Write short note on Washing Machine.	07
	(b)		07
		two non-degenerate form.	
		$F(w,x,y,z) = \Sigma (1,4,6,7,8,9,10,11,15)$	
05	(-)	OR Write short note on Dhoteconier mechine	07
Q.5	(a)		07 07
	(b)	(i) Clocked R-S flip-flop (ii) JK flip-flop	07
		(i) Clocked K-5 inp-inop (ii) iK inp-inop *******	