## GUJARAT TECHNOLOGICAL UNIVERSITY BE- V<sup>th</sup> SEMESTER-EXAMINATION - MAY/JUNE - 2012 ode: 151703 Date: 05/06/2012

U			ate: 05/06/2012	
Subject Name: Electronics in Industries  Fime: 02:30 pm - 05:00 pm  Instructions:  1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks.			l Marks: 70	
Q.1	(a)	The internal resistance for a UJT are $R_{B1}$ = 7 K $\Omega$ and $R_{B2}$ =3 K $\Omega$ . Calculate the intrinsic stand-off ratio. If externally applied voltage $V_{BB}$ is 30V, Calculate the stand-off voltage.	07	
	<b>(b)</b>	Explain full-wave bridge rectifier with resistive-inductive load.	07	
Q.2	(a)	Explain Schottky diode with cross sectional view, symbol and plot of characteristic.	07	
	<b>(b)</b>	Describe enhancement type MOSFET.  OR	07	
	<b>(b)</b>	Explain BENISTOR with its basic structure and characteristic.	07	
Q.3	(a) (b)	Explain three layer and five layer DIAC.  Describe silicon controlled switch in detail.  OR	07 07	
Q.3	(a)	Write a note on thyristor with cross sectional view, symbol and plot of characteristic.	07	
	<b>(b)</b>	Introduce new trends in power semiconductor devices.	07	
Q.4	(a)	A voltage, 220 sin $(2\pi 50t)$ is applied to a half-wave rectifier with load resistance of 10 K $\Omega$ . Calculate the maximum current, rms current, average current, ac power input, dc power output and ripple factor.	07	
	<b>(b)</b>	Discuss operation, circuit symbol and characteristic of programmable unijunction transistor.	07	
0.4	(2)	OR Write a note on Jones commutation.	07	
Q.4	(a) (b)	With necessary circuit diagram explain overcurrent protection of power semiconductor devices.	07 07	
Q.5	(a)	A three-phase half-wave controlled rectifier is connected to a 230V and 50 Hz input supply with a 200 $\Omega$ load resistance. If the desired average output voltage is 25 % of the maximum possible average output voltage, calculate the delay angle $\alpha$ .	07	
	<b>(b)</b>	Explain the operation of a three phase fully-controlled bridge rectifier. <b>OR</b>	07	
Q.5	(a) (b)	Describe dual converter using circuit diagram and waveforms. Explain mid-point configuration with resistive load for full wave controlled rectifiers.	07 07	
		******		