Seat N	lo.: _	Enrolment No		
		GUJARAT TECHNOLOGICAL UNIVERSITY		
BE- VII <sup>th</sup> SEMESTER-EXAMINATION – MAY/JUNE- 2012			<i>-</i> /2012	
Subject code: 170906 Subject Name: Advanced Power Electronics-I Time: 02:30 pm – 05:00 pm			Date: 29/05/2012	
			Total Marks: 70	
Instructions:			iarks: /u	
		empt all questions.		
		ke suitable assumptions wherever necessary.		
3.	Figu	ures to the right indicate full marks.		
Q.1	(a)	Explain diode clamped 3-level inverter configuration. Draw gate signals and inverter terminal voltage of one phase.	07	
	<b>(b)</b>	Discuss L type ZCS resonant inverter with neat circuit diagram and waveform.	07	
Q.2	(a)	Draw circuit diagram and output voltage phasor diagram of 12-pulse converter. Explain 5 <sup>th</sup> and 7 <sup>th</sup> harmonics elimination in 12-pulse converter.	07	
	<b>(b)</b>	Draw circuit diagram of single phase multilevel cascaded H bridge inverter. Explain its working principle and mention its features, advantages and limitations.	07	
		OR		
	<b>(b)</b>	Explain flying capacitors multilevel inverter topology. Compare it with other multilevel inverter topologies.	07	
Q.3	(a)	Explain concept, advantages and limitations of multi-pulse converter. How reduction in harmonics in output voltage can be achieved?	07	
	<b>(b)</b>	With neat circuit diagram and waveform discuss class E resonant inverter.  OR	07	
Q.3	(a)	Discuss various transformer connections for multi-pulse converter.	<b>07</b>	
	<b>(b)</b>	Discuss series resonant inverter with neat circuit diagram and waveform.	07	
Q.4	(a)	Discuss push pull converter and its application in dc power supply.	07	
C.	<b>(b)</b>	With neat circuit diagram explain resonant dc power supply.  OR	07	
<b>Q.4</b>	(a)	Draw block diagram of UPS and discuss each block in detailed.	07	
	<b>(b)</b>	With neat circuit diagram explain resonant ac power supply.	07	
Q.5	(a)	Discuss stepper motor control strategy with appropriate diagram.	07	

\*\*\*\*\*\*

(b) What do you mean by electronically commutated motors? Discuss 07

(b) Discuss control of brushless dc drive. Give its applications.

switching circuit of BLDC motor drive.

(a) Discuss energy conversion process in SRM. Give its applications.

Q.5

**07** 

**07**