## GUJARAT TECHNOLOGICAL UNIVERSITY BE- VII<sup>th</sup> SEMESTER-EXAMINATION - MAY/JUNE- 2012

Subject code: 172403 Date: 09/0		ect code: 172403 Date: 09/06/2012	
\$	Subje	ect Name: Power Processing Circuits II	
		: 02:30 pm – 05:00 pm Total Marks: 70	
]		ructions:	
	2.	Attempt all questions.  Make suitable assumptions wherever necessary.  Figures to the right indicate full marks.	
Q.1	(a) (b)	Explain the battery charging process and Ampere-Hour calculation for battery. Explain ON-Line and OFF-Line UPS with block diagram.	07 07
Q.2	(a) (b)	Draw the schematic of active front-end rectifier. List its advantages and applications. List the performance parameters of inverter. Explain the working of single-phase full-bridge inverter with circuit diagram and waveforms.  OR	07 07
	<b>(b)</b>	Explain the working principle of single-phase half-bridge inverter with circuit diagram and waveforms. List domestic and industrial applications of inverters.	07
Q.3	(a) (b)	Explain the current source inverter with circuit diagram and waveforms.  Explain the 120° conduction mode of three-phase inverter with circuit diagram and waveforms.  OR	07 07
Q.3	(a)	Explain the modified Mc-Murray half-bridge inverter with circuit diagram and waveforms.	07
	<b>(b)</b>	Explain the working of three-phase series inverter with neat circuit diagram.	07
Q.4	(a)	Explain zero-voltage switching resonant converter with circuit diagram and waveforms.	07
	<b>(b)</b>	Explain the diode-clamped 5-level multilevel inverter with circuit diagram and waveforms.	07
Q.4	(a)	OR Explain features of multilevel inverter. List applications of multilevel inverter and explain any one in detail.	07
	<b>(b)</b>	With the help of circuit diagram and waveforms explain the two-stage sequence control of ac voltage controllers with R and RL load.	07
Q.5	(a)	Explain the working of three-phase to single-phase cycloconverter with circuit diagram and waveforms.	07
	<b>(b)</b>	Explain the Sinusoidal PWM technique of the voltage control of inverter with waveforms and equations.	07
Q.5	(a) (b)	OR  Explain the voltage control of inverter with output side control techniques.  Explain phase dead-banding with modulation reference waveforms. Explain triplen injection modulation.  ***********************************	07 07
		ላ ላ ላ ላ ላ ላ ላ ላ ላ ላ ላ ላ ላ ላ ላ ላ	

1