Seat No.: _

Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III(OLD) • EXAMINATION - WINTER 2016

Subject Code:130901

Subject Name: Circuits and Networks

Date:04/01/2017

Time:10:30 AM to 01:00 PM

Total Marks: 70

- Instructions:
 - 1. Attempt all questions.
 - 2. Make suitable assumptions wherever necessary.
 - 3. Figures to the right indicate full marks.
- Q.1 (a) Define Kirchhoff's Current Law and determine all mesh currents of a network 07 which is shown in Figure -1.
 - (b) Define Kirchhoff's Voltage Law and determine current i in the network using 07 node voltage analysis. The network is shown in Figure -2.
- Q.2 (a) State the Norton's Theorem. Show the mathematical steps to find out the load 07 current of given network using Norton's theorem.
 - (b) Determine current passing through ammeter (R_A = 2 ohm) connected in the **07** whetstone bridge. Use Thevenin's Theorem for the electrical network shown in Figure 3.

OR

- (b) For the network shown in Figure 4, determine the value of R_L to that will or cause the power in R_L to have maximum value. What will be the value of power under this condition?
- Q.3 (a) Using definition, determine the Laplace transform of the following time 07 domain functions.

(1) $f(t) = t^3$ (2) $f(t) = \sinh(wt)$

(b) Explain the significance of poles and zeros. Determine the poles and zeros of 07 the following function and show the plot pole-zero diagrams for the same.

OR

- **Q.3** (a) Find $i(0^+)$, $di/dt(0^+)$ and $d^2i/dt^2(0^+)$ for the network shown in Figure 5. The **07** switched is moved from position 1 to position 2 at t=0.
 - (b) Prove the following property of Laplace Transform. 07[df(t)]


$$1.L\left[\frac{df(t)}{dt}\right] = sX(s-x(0))$$
$$2.L\left[\int_0^t x(t)dt\right] = \frac{X(s)}{s}$$

- Q.4 (a) State Millman's Theorem. Prove this theorem with considering electrical 07 network.
 - (b) Figure 6 shows mutually coupled network. Draw the dot equivalent network 07 and write the KVL equations for the same.

- Q.4 (a) Determine the step (DC) response of R-C series circuit. Also draw the current 07 transient response curve for the same.
 - (b) In the network of Figure 7, a steady state is reached with the switch K open. 07 At t=0, the switch is closed. Determine i(t) for t>0.
- Q.5 (a) Explain the procedure to find out ABCD parameters of any given two port 07 network. Also discuss the significance of each parameter.
 - (b) Derive the relationship between Z parameters in terms of Y Parameters for 07 two port network.

OR

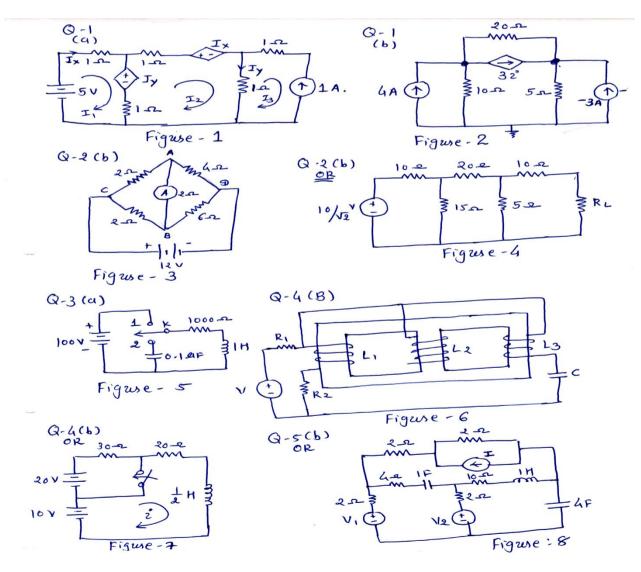- **Q.5** (a) Define the following terms.
 - 1. Oriented Graph2. Sub graph3. Tree4. Twigs5. Links6. Co-tree
 - (b) For the network shown in Figure 8, draw the oriented graph and write (i) 07 Incidence matrix (ii) tieset matrix and (iii) f-cutset matrix. Also draw the oriented graph.



2

07