Date:06/01/2017

**Total Marks: 70** 

# **GUJARAT TECHNOLOGICAL UNIVERSITY**

# **BE - SEMESTER-III(OLD) • EXAMINATION - WINTER 2016**

Subject Code:131101

Subject Name:Basic Electronics Time:10:30 AM to 01:00 PM

## Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Define
  - (i) Potential energy
  - (ii) Electron volt
  - (iii) *hole* in semiconductor
  - (iv) Space charge region
  - (v) Diffusion capacitance of diode
  - (vi) Photovoltaic Effect
  - (vii) The Continuity Equation
  - (b) Draw and explain volt-ampere characteristic of an avalanche diode. What is meant by *cut in* voltage and reverse saturation current? what is effect of temperature on these two parameters?
- Q.2 (a) (i) Draw the steady state output voltage waveform with respect to input 07 voltage  $V_i$ = 5 sin  $\omega t$  for Figure 1(a) and Figure 1(b)

(ii) Compare half wave, center tapped and bridge rectifier

(b) What is comparator circuit? How does such a circuit differ from a clipping 07 circuit?

OR

- (b) Define current gain  $\alpha$  and  $\beta$  for transistor. Derive relationship between  $\alpha$  and  $\beta$ .
- Q.3 (a) (i) Compare CB, CE and CC configuration in transistor. (ii) Explain Early effect and Reach through condition related to transistor.
  - (b) Give the complete analysis of a transistor amplifier circuit using h parameters. 07 Find current gain and voltage gain in terms of h parameters.

#### OR

- Q.3(a)Discuss various biasing methods of FET.07(b)(i) Explain : Phototransistor07(ii)Explain : Alloy type transistor construction07Q.4(a)Explain bias compensation circuits for transistor in detail07
  - (b) Explain the basic structure of n channel field effect transistor. Explain its **07** operation.

## OR

- Q.4 (a) What is thermal run away in transistor? Define thermal resistance. What 07 should operating point consideration to minimize self heating in transistor?
  - (b) Explain structure, the drain characteristic and the transfer curve of p channel **07** enhancement type MOSFET. Define threshold voltage.
- Q.5 (a) Explain why even harmonics are not present in a push pull amplifier. give 07 additional advantages of this circuit over that of a single transistor amplifier.

07


07

(b) Determine the quiescent current and collector to emitter voltage for a silicon transistor with  $\beta$ =50 in the self bias method (Figure 2), the circuit component values are

 $V_{cc}=20 V$   $R_{c}=2 K\Omega \text{ (Collector Resistor)}$   $R_{1}=100 K\Omega$   $R_{2}=5 K\Omega$  $R_{e}=0.1K\Omega \text{ (Emitter Resistor)}$ 

### OR

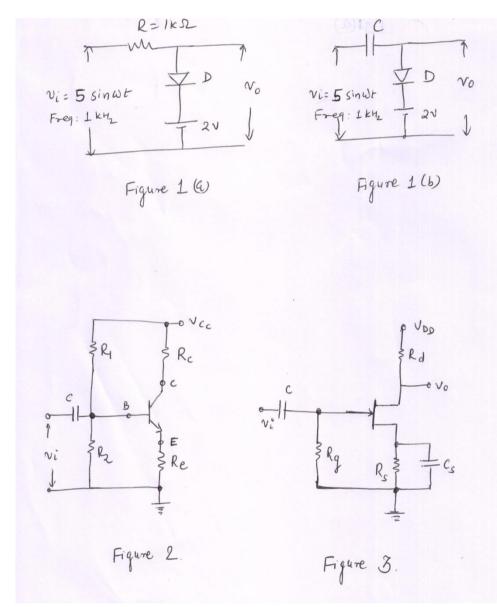- Q.5 (a) What is cross over distortion in class B push pull amplifier. How this problem 07 can overcome, discuss with suitable circuit diagram.
  - (b) For source self bias circuit shown in Figure 3, utilized an *n* channel FET for which  $V_p$ = -2 V and  $I_{DSS}$ =1.65 mA. It is desire to bias the circuit at  $I_D$ =0.8 mA using  $V_{DD}$ =24 V. Find  $V_{GS}$ ,  $g_m$  and  $R_s$



\*\*\*\*\*