GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-IV(OLD) • EXAMINATION - WINTER 2016			
Subject Code:142402 Date:24/11/			16
Subject Name: Fundamentals of Power Electronics			
	Time:02:30 PM to 05:00 PM Total Marks: 70		
Instructions:			
	1. 2. 3.	I J	
Q.1	(a)	With the help of neat block diagram, explain the functional elements of power electronics system.	07
	(b)	Draw the V-I characteristics of TRIAC and explain its working principle.	07
Q.2	(a)	Draw symbols and V-I characteristics of (a) Diode (b) DIAC (c) BJT (d) LASCR (e) IGBT (f) MOSFET (g) SCR	07
	(b)	Write a detail note on:- TURN ON methods of SCR. OR	07
	(b)	Explain dv/dt and di/dt protection of SCR	07
Q.3	(a) (b)	Draw & explain Power circuit and transient response of Fast recovery diode. Draw the V-I characteristics of UJT and explain its working principle. OR	07 07
Q.3	(a)	Compare between voltage source inverter(VSI) and current source inverter (CSI)	07
	(b)	Explain in detail Class-A Commutation with necessary waveforms	07
Q.4	(a)	Explain with necessary circuit and waveforms the working of single-phase half wave controlled rectifier with R load.	07
	(b)	Explain the basic principle of operation of cycloconverter with a neat equivalent circuit diagram.	07
0.4	(c)	OR Discuss principle and working of SMPS with the help of block diagram.	07
Q.4	(a) (b)	With the help of circuit diagram, explain the working of step down chopper.	07 07
Q.5	(a)	Draw and explain single phase bridge inverter with necessary circuit and waveform.	07
	(b)	Draw and explain single phase MC-MURRAY Inverter circuit with voltage and current waveforms.	07
OR			
Q.5	(a)	Describe the operation of $1-\emptyset$ half wave a. c voltage regulator with the help of voltage and current waveform.	07
	(b)	Compare 1-phase & 3-phase uncontrolled rectifier.	07
