| Seat No.: | Enrolment No |
|-----------|--------------|
| Jean 110  | Emoment No   |

## GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER- V • EXAMINATION – WINTER 2016

Subject Code: 151003 Date: 24/11/2016 **Subject Name: Integrated Circuits and Applications** Time: 10:30AM – 01:00PM **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. 0.1 (a) What are the types of comparator? Explain the operation of an inverting **07** comparator using op-amp. with the help of input and output waveforms. Enlist the applications of comparator. **(b))** Explain working of monostable multivibrator using IC 555 with internal 07 blocks and waveforms. write applications of it. 0.2 07 Draw and explain circuit diagram of instrumentation amplifier using transducer (a) bridge and op-amp. Enlist the applications of it. Draw and explain Triangular and Saw tooth wave generator circuit using op-07 **(b)** amp. OR Explain the operation of first order Butterworth low-pass filter with the help of 07 circuit diagram, derivation and waveforms. **Q.3** Explain wide band-pass filter with necessary circuit, derivation and 07 (a) waveforms. State the applications of operational transconductance amplifier and explain 07 any one with necessary circuit and derivations. OR What is PLL? Explain operation of PLL with basic blocks and mention any 0.3 07 four applications of it in radio communication. Write short note on: (i) Zero Crossing Detector **07 (b)** (ii) Peak Detector

| Q.4 | (a)        | Draw the circuit of basic differentiator using an op-amp. What are the problems associated with this configuration? How they are overcome?                              | 07 |
|-----|------------|---|----|
|     | <b>(b)</b> | Design a circuit using Operational amplifier in non- Inverting configuration that will give sum of three different input voltages.                                      | 07 |
|     |            | OR  |    |
| Q.4 | (a)        | Derive the expression for voltage gain , input resistance, output resistance and bandwidth of an inverting amplifier using op-amp with negative voltage shunt feedback. | 07 |
|     | <b>(b)</b> | Draw clamper circuit using op-amp. and explain operation of it with the help of necessary waveforms   | 07 |
| Q.5 | (a)        | Write short note on: Monolithic Power Amplifier (LM380)   | 07 |
|     | <b>(b)</b> | Explain working of Free Running Ramp Generator with necessary circuit and waveforms.  | 07 |
|     |            | OR  |    |
| Q.5 | (a)        | Draw and explain the circuit of practical inverting integrator using an op-amp. with necessary derivations.   | 07 |
|     | <b>(b)</b> | Give classification of filters with four basic types. Discuss importance of magnitude and frequency scaling in filter design.   | 07 |

\*\*\*\*\*

\*\*\*\*\*\*