| Seat No.: | Enrolment No. |
|-----------|---------------|
| Seat 110 | Emonitent No |

Subject Code: 162405

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER - VI (OLD).EXAMINATION - WINTER 2016

Date: 24/10/2016

| | • | ect Name: Power Processing Circuits - I : 10:30 AM to 01:00 PM Total Marks: 70 etions: | |
|-----|------------|--|----------|
| | | Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. | |
| Q.1 | (a) (b) | | |
| Q.2 | (a) (b) | Explain working of Morgan's chopper with circuit diagram & waveforms. Draw basic block diagram of switch mode power supply. Discuss full-bridge topology of DC-DC converter with necessary diagrams. OR | 07 07 |
| | (b) | Explain Push-pull converter type DC-DC isolated converter with necessary diagram & waveforms. Derive equation for O/P voltage. | 07 |
| Q.3 | (a) | Define following terms with respect to DC power supply. 1. Supply Voltage 2. Noise 3. Regulation 4. Supply Current 5. Efficiency 6. Physical dimensions 7. Load voltage | 07 |
| | (b) | Explain 3-Phase, 3-Pulse uncontrolled rectifier with circuit diagram & waveforms. Consider load is Resistive. | 07 |
| Q.3 | (a) | OR Give comparison between Linear Regulated Power Supply & Switch Mode Power | 07 |
| | (b) | Supply. Explain 3-Phase, 6-Pulse uncontrolled rectifier with circuit diagram & waveforms. Consider load is RL type. | 07 |
| Q.4 | (a) | A boost regulator has following parameters: $V_{in} = 5V$, $V_o = 15V$, $I_o=0.5A$ & Switching Frequency = 25KHz. If L=150uH & C=220uF, Determine (1) Duty Cycle (2) Ripple Current of & Peak current of L (3) Critical values of L & C. | 07 |
| | (b) | Discuss various control strategy used in DC-DC converter (Chopper). OR | 07 |
| Q.4 | (a) | Discuss Single Ended Primary Inductor Converter with necessary circuit diagram & waveforms. | 07 |
| | (b) | Explain operation of four quadrant chopper with necessary operational diagram. | 07 |
| Q.5 | (a) | Describe operation of 1-phase semi-converter circuit diagram with RL load in continuous & discontinuous mode. | 07 |
| | (b) | Discuss working of Forward converter (DC-DC). Also discuss benefits of tertiary windings. | 07 |
| Q.5 | (a) | OR Explain effect of source inductance in 1-phase full controlled converter. Draw | 07 |
| _ | (b) | necessary diagrams & waveforms in support to your answer. Write a short note on Luo converter. | 07 |
| | | | |
