GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-VII(OLD) • EXAMINATION – WINTER 2016

Subject Code: 172401 Date: 25/11/201 Subject Name: Power Electronics Systems Modelling			
]	•	10:30 AM to 01:00 PM Total Marks: 70	
		 Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. 	
Q.1	(a) (b)	State differences between single input single output and multi input multi output system. Obtain transfer function of separately exited DC shunt motor operated with armature voltage control.	07 07
Q.2	(a)	Draw and Explain the block diagram of Power Electronics System with reference to modelling.	07
	(b)	Obtain mathematical model of DC motor.	07
		OR	07
	(b)	Explain DC motor speed control.	07
Q.3	(a)	Develop State-space model of the Buck-Boost converter.	07
	(b)	Explain DC transformer model with necessary equations and figures OR	07
Q.3	(a)	Explain Controllability and Observability of the system with suitable example.	07
	(b)	What is normalization? State its importance.	07
Q.4	(a)	What do you mean by small signal approximation? Explain with appropriate example.	07
×	(b)	Obtain state space model of parallel R-L-C circuit.	07
		OR	
Q.4	(a)	Explain the difference between ideal and physical models of AC transformer. Draw neat diagrams.	07
Q.4	(b)	Explain the state space model of a full bridge inverter.	07
Q.5	(a)	Explain the modelling of PWM inverter.	07
X .0	(b)	Draw and explain the modelling of PWM inverter.	07
Q.5	(a)	Find out the steady state output voltage for a buck chopper using small-ripple approximation. Draw necessary diagrams & waveforms. Also derive the equation for voltage conversion ratio $M(D)$ and draw it's graph	07
	(b)	voltage conversion ratio M(D) and draw it's graph. What is Canonical Circuit Model? Explain the manipulation of buck-boost converter model into canonical form.	07
