GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-VII(OLD) • EXAMINATION – WINTER 2016

Subject Code: 172403Date: 23/11/2016Subject Name: Power Processing Circuits - IITime: 10:30 AM to 01:00 PMTime: 10:30 AM to 01:00 PMTotal Marks: 70Instructions:Total Marks: 70)16
mst		Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. Notations/ symbols used have usual meanings.	
Q.1	(a)	Explain following terms w.r.t.an inverter:- Performance parameters, applications, limitations.	07
	(b)	Why battery is required? Enlist various methods for battery charging and explain any one in detail.	07
Q.2	(a) (b)	Describe the operation of a parallel resonant pulse inverter in detail. $v_s = \sqrt{2}v_s \sin wt$	07 07
	(b)	Fig 1 Analyze the working of circuit shown in Fig1. OR With waveforms, explain the operation of a 1-Ø to 1-Ø cyclo-converter.	07
Q.3	(a) (b)	Discuss Trapezoidal PWM technique for inverter control. Explain diode clamped multi-level inverter in brief.	07 07
Q.3	(a) (b)	OR Describe input side voltage control technique for inverter using un-controlled rectifier and chopper. Explain cascaded H – bridge multi-level inverter in brief	07 07
Q.4	(a) (b)	Discuss the Phase angle control. w.r.t AC controller. Write short note on :- Active front-end rectifier. OR	07 07
Q.4	(a) (b)	With waveforms, explain the operation of a 3-Ø cyclo-converter. Write short note on :- Single phase static switch.	07 07
Q.5	(a) (b)	Explain the basic principle of operation of an off-line UPS. Give circuit analysis of CSI with resistive load. OR	07 07
Q.5	(a) (b)	Discuss utility of A-H rating of a battery. Discuss Triplen harmonic injection technique for inverter control.	07 07
