Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER - VIII.EXAMINATION - WINTER 2016

	•	ect Code: 182401 Date: 21/10/2016 ect Name: Power Electronics Applications in Power System	
T	ime	tions: 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks.	
Q.1	(a) (b)	Discuss basic elements of static relay with illustration. Enlist the advantages of static relays over electromagnetic relays. Also specify the limitation of static relays.	07 07
Q.2	(a)(b)	Explain the principle of shunt compensation with necessary diagram and waveform. Discuss Improved single-phase utility Interface. OR	07 07
	(b)	Discuss Interface for a bidirectional power flow.	07
Q.3	(a)	Discuss various possible HVDC configuration employed in the transmission system.	07
	(b)	Explain the typical converter system used in HVDC Transmission. OR	07
Q.3	(a) (b)	Compare FACTS controller with HVDC Transmission. Discuss various types of FACTS controller and its advantages.	07 07
Q.4	(a) (b)	Explain the operation of TCR. Explain the operation of STATCOM.	07 07
Q.4	(a) (b)	OR Explain the operation of TSC. Explain the operation of SVC.	07 07
Q.5	(a)	Draw and explain static distance relay drawing various waveforms seen at the	07
	(b)	output of each block. Draw and explain the static IDMTL over current relay. OR	07
Q.5	(a)	Illustrate the interconnection of renewable energy source and energy storage	07
	(b)	system to utility grid. Explain photovoltaic array interconnections.	07
