Seat No.:	E 1 M .
Seat NO.	Enrolment No.

## GUJARAT TECHNOLOGICAL UNIVERSITY

BE SEMESTER 1st / 2nd (NEW) EXAMINATION WINTER 2016 Subject Code: 2110016 Date: 25/01/2017 **Subject Name: Basic Electronics** Time:10:30 AM TO 1:00 PM **Total Marks: 70 Instructions:** 1. Question No. 1 is compulsory. Attempt any four out of remaining Six questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. MARKS **Q.1 Objective Question (MCQ)** Choose an appropriate option from the following: 07 (a) 1. In an Electrical system, the flow of current follows: (a) De Morgan's law (b) Boyle's law (c) Curie's law (d) Ohm's law 2. The equivalent octal of the binary number (101010101011)<sub>2</sub> is (a)  $(5352)_8$  (b)  $(2523)_8$  (c)  $(5253)_8$  (d)  $(225253)_8$ X(t) = -X(t) is the property of **3.** (a) Even signal (b) Odd signal (c)Periodic signal(d) Aperiodic signal 4. If a 1 Hz square signal is given to a bulb, how long will it glow? (a) 1second (b) 2 second (c) 0.5 second (d) 0 second The inductance offered by a inductor of 1 H to a DC signal is 5. (a) 0 (b) infinity (c) 1 (d) indeterminate Following gates are known as Universal Logic Gates 6. (a) AND, OR (b) NAND, NOR (c) AND, NOR (d) NAND, OR A circuit that converts AC signal to DC signal is known as a 7. (a) Rectifier circuit (b) Inverter circuit (c) RL circuit (d) RC circuit Choose an appropriate option from the following: 07 **(b)** The IC 741 Operational Amplifier cannot: 1. (a) Add signals (b) Subtract signals (c) Transform signal (d) Differentiate signal 2. A Flip Flop has got a memory of (a) 1 bit (b) 2 bit (c) 4 bit (d) 8 bit **3.** An operational amplifier IC 741 has got (a) 2 inputs, 1 outputs (b) 1 inputs, 2 outputs (c) 1 input 1 output (d)2 inputs, 2 outputs Wireless mobile cells are \_\_\_\_\_\_ in shape 4. (a) pentagon (b) hexagon (c) circular (d) square 5. A system is linear if \_\_\_\_\_ is true. (a) KVL (b) KCL (c) Superposition theorem (d) Ohm's law PAM stands for 6. (a) Pulse And Modulation (b) Pulse Analog Modulation (c) Pulse Altitude Modulation (d) Pulse Amplitude Modulation A control system with feedback has 7. (a) maximum error (b) minimum error(c)zero error (d) infinite error **Q.2** Define Resistor. Quote all the characteristics of any resistor. If you 03 go to the market to purchase a resistor, apart from resistance what else will you quote so that the safety is ensured? **(b)** How does a Voltmeter differ from an Ammeter? 04 (c) What is Superposition Theorem? Prove the same for a network. **07** 

(a) Draw an inverting amplifier and write the equation for its gain.

(c) Explain the working of a band pass filter. Find out its bandwidth.

(b) Show a Low Pass Filter. Define the higher frequency cutoff.

03

04

07

**Q.3** 

Q.4	(a)	Assign a binary code to all the 52 playing cards. Use minimum number of bits.	03
	<b>(b)</b>	State and Prove De Morgan's laws.	04
	(c)	Design an Op-amp based circuit that does the following $V_0=V_1-2*V_2$ .	07
Q.5	(a)	Draw an SR Flip Flop. Plot its truth table and Symbol.	03
	<b>(b)</b>	Draw the block diagram of a multiplexer circuit and label the pins.	04
	(c)	How does a PAM signal differ from a PWM, PPM signal?	07
(lt	(a)	Draw the ISO- 7 layer block diagram for Computer Network	03
	<b>(b)</b>	Define Antenna, Waveguide, Transmission Lines and Flux density.	04
	(c)	Draw the block diagram of a Communication system. Explain each block.	07
`_	(a)	Define a control system. Classify them and state their advantages.	03
	<b>(b)</b>	Explain Frequency Reuse in Cellular Communication	04
	(c)	Discuss the types of Computer Networks.	07

\*\*\*\*\*