Seat No.: \_ Enrolment No. **GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-III(New) • EXAMINATION - WINTER 2016** Subject Code:2130305 Date:06/01/2017 Subject Name: Analog Circuits-I Time: 10:30 AM to 01:00 PM **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. MARKS **Q.1 Short Questions** 14 1 What circuit activity may shift a characteristic curve so that diode operating points are different? (a) higher power (heat) (c) lower voltage (b) higher resistance (d) lower current In a power supply diagram, which block indicates a smooth dc output? 2 (a) Transformer (c) rectifier (b) Filter (d) regulator With a half-wave rectified voltage across the load resistor, load current 3 flows for what part of a cycle? (a) 0 degrees (c) 180 degrees (b) 90 degrees (d) 360 degrees When transistors are used in digital circuits they usually operate in the: 4 (c) saturation and cutoff regions (a) active region (b) breakdown region (d) linear region What is the current gain for a common-base configuration where  $I_E =$ 5  $4.2 \text{ mA} \text{ and } I_{C} = 4.0 \text{ mA}?$ (a) 16.80 (c) 0.20

**6** Which is beta's current ratio?

(b) 1.05

which is belas current ratio?	
(a) $I_C/I_B$	(c) $I_B/I_E$
(b) $I_C/I_E$	(d) $I_E/I_B$

7 Which is the higher gain provided by a C-E configuration?

(a) Voltage	(c) resistance
(b) Current	(d) power

**8** A "U" shaped, opposite-polarity material built near a JFET-channel center is called the:

(d) 0.95

(a) Gate	(c) drain
(b) Block	(d) heat sink

- **9** When a number of stages are connected in parallel, the overall gain is the product of the individual stage gains.
  - (a) True (b) false

**10** A Schmitt trigger is

- (a) a comparator with only one trigger point.
- (b) a comparator with hysteresis.
- (c) a comparator with three trigger points.
- (d) none of the above.

	11	In $a(n)$ when the input voltage eveneds a specified reference		
	11	In a(n), when the input voltage exceeds a specified reference voltage, the output changes state.		
		(a) Integrator (c) differentiator		
		(b) summing amplifier (d) comparator		
	12	What is the Output of to integrator if the input is Step signal?		
	13	An op-amp has an open-loop gain of 90,000. $V_{sat} = \pm 13$ V. A differential voltage of 0.1V <sub>p-p</sub> is applied between the inputs. What is the output voltage?		
		(a) $13 V$ (c) $-13 V$ (b) $13 V_{p-p}$ (d) $26 V_{p-p}$		
	14	Define CMRR.		
Q.2	<b>(a)</b>	How to calculate bulk resistance?	03	
	<b>(b)</b>	Explain V-I characteristics of Diode.	04	
	(c)	Explain Bridge rectifier in detail.	07	
		OR		
	(c)	Explain Zener diode with its applications.	07	
Q.3	<b>(a)</b>	Draw circuit diagram of Positive and Negative Bias Series Clipper.	03	
	<b>(b)</b>	Explain Scaling amplifier with three inputs using OP-Amp.	04	
	(c)	Explain close–loop non-inverting configuration of OP-Amp.	07	
01		OR	0.2	
Q.3	(a)	Explain positive Clamper circuit.	03	
	<b>(b)</b>	Explain input-output characteristics of CB configuration of BJT.	04	
~ .	(c)	•	07 03	
Q.4	(a)	series feedback.		
	(b)	-	04	
	( <b>c</b> )	Describe construction and working of Depletion Mode MOSFET. <b>OR</b>	07	
Q.4	(a)	Differentiate between Enhancement and Depletion mode MOSFET.	03	
	<b>(b)</b>	Describe application of open-loop configuration of OP-Amp.	04	
	(c)	Write short note on Differentiator.	07	
Q.5	(a)	In the inverting configuration of summing amplifier, Va=1V, Vb=2V, Vc=3V, Ra=Rb=Rc=3k\Omega, Rf=1k $\Omega$ , and supply voltage =±15V. determine output voltage Vo.	03	
	(b)	In the Astable multivibrator, $R_A=2.2k\Omega$ , $R_B=3.9k\Omega$ , and $C=0.1\mu$ F.Determine the positive pulse width $t_c$ , negative pulse width $t_d$ , and free-running frequency $f_0$ .	04	
	(c)	Write short note on Sample and hold circuit.	07	
		OR		
Q.5	(a)	In the non-inverting configuration of summing amplifier, Va=2V, Vb=4V, Vc=6V, Ra=Rb=Rc=1k\Omega, Rf=4k\Omega, R1=2k\Omega and supply voltage = $\pm 15V$ . determine output voltage Vo.	03	
	<b>(b)</b>	Explain Astable Multivibrator work as Square wave generator.	04	
	(c)	Explain Log and Antilog amplifier using OP-Amp.	07	
	. /			

\*\*\*\*