Seat No.: GUJARAT TECH		: Enrolment No			
		GUJARAT TECHNOLOGICAL UNIVERSITY			
		<b>BE - SEMESTER-III(New) • EXAMINATION - WINTER 2016</b>			
Sub	Subject Code:2130902 Date:0				
Sub	iect	Name:Analog Electronics			
Time: 10:30 AM to 01:00 PM Total Markey					
linet	. I		.3.70		
Inst	ruct	ions:			
•	• A	ttempt all questions.			
•	• N	lake suitable assumptions wherever necessary.			
	• Fi	gures to the right indicate full marks.			
			MARKS		
0 1		Short Questions	14		
Q.1	1	Short Questions What is the position of Q point on the load line for Class AP amplifier?	14		
	T	what is the position of Q-point on the load line for class AB ampliner?			
	2	In which negative amplifiers the in-put resistance is increases?			
	3	Define: CMRR			
	4	Define: Slew Rate.			
	5	Draw the OP-AMP based subtractor circuit.			
	6	Which component is used as feed back element for differentiator?			
	7	Write the condition for sustained oscillator?(Barkhausen criteria)			
	8	What is the value of Hysteresis voltage for Schmitt trigger circuit?			
	9	Define Q of a filter.			
	10	Draw the pin diagram of IC 555.			
	11	Which multivibrator is used as a flip flop?			
	12	How much voltage is generated by the IC 7812?			
	13	Define VCO.			
	14	Define setting time.			
Q.2	(a)	Explain the basic principal of feed back.	03		
	(b)	Compare: Class B Push pull and Complementary symmetry type of power amplifier.	04		
	(c)	Explain in detail: Class B push pull amplifier.	07		
		OR			
	(c)	Draw the C.E. amplifier circuit with and without bypassed R <sub>E</sub> , also draw the hybrid	07		
0.2	(2)	equivalent circuit for the same.	02		
Q.5	(a)	on-amp whose slew rate is 11//uS	05		
	(b)	Derive the equation for non inverting amplifier using OP-AMP	04		
	(~) (c)	Explain the working of a summing and averaging amplifier when connected in	07		
	(-)	inverting mode.	•••		
		OR			
Q.3	(a)	For inverting amplifier V1= 1V, V2= 3V, V3= 2V with R1=R2=R3= 2K\Omega and RF= 3K\Omega,	03		
		determine the output voltage.			
	(b)	Compare: inverting and non inverting amplifier.	04		
	(c)	Explain in detail voltage follower with its applications.	07		
Q.4	(a)	Compare: R-C phase shift and wein bridge oscillator.	03		
	(a)	Design a K-C phase shift oscillator to produce a sinusoidal output at 1K <sub>HZ</sub> , using	04		
	(c)	Capacitor value 0.01 μF. Write short note on : Integrator	07		
	(5)	white short note on a megration.			

OR

Q.4	(a) (b)	Explain inverting comparator. Compare: Comparator and Schmitt trigger.	03 04
	(c)	Explain symmetric Square wave generator using op-amp.	07
Q.5	(a)	Design a monostable multivibrator using IC 555 for V <sub>cc</sub> = 12V and pulse width of 1ms, and capacitor = $0.1\mu$ F.	03
	(b)	Compare: Astable, monostable and bistable Multivibrator.	04
	(c)	Explain in detail: first order butter worth low-pass filter.	07
		OR	
Q.5	(a)	List out the different performance parameter of a power supply.	03
	(b)	Describe the operation of a LM 317 voltage regulator.	04
	(c)	Describe the basic building blocks of PLL.	07

\*\*\*\*\*