Subjec	et Co	Enrolmen GUJARAT TECHNOLOGICAL UNIVER BE - SEMESTER-IV(New) • EXAMINATION – WINTI ode:2141003 nme:Electronics Measurement and Instruments 0 PM to 05:00 PM	RSITY	
	1. A 2. M	ttempt all questions. Take suitable assumptions wherever necessary. Egures to the right indicate full marks.		
				MARKS
Q.1		Short Questions		14
Q.1	1	What is Electronic Instrument?		14
	2	Define Accuracy and Sensitivity of instrument.		
	3	Define the term null as it applies to bridge measurement.		
	4	Which bridge circuit is used for measurement of low resista	ince?	
	5	The measure value of inductor is 25.3 mh and true value is . Find the relative error.	21.4 mh	
	6	How do the X-shift and Y-shift function of CRO?		
	7	What is the criteria for balance of a Wheatstone bridge?		
	8	Define Transducer.		
	9	What is range of counting for 4 and 1/2 digit display?		
	10	What is operating principle of temperature transducer?		
	11	Define term Isolation.		
	<b>12</b>	What is Hall effect principle?		
	13	List out disadvantages of Digital Instrument.		
	14	Which Bridge circuit is used for measurement of capacitor?	<b>)</b>	
Q.2	(a)	Define and explain Systematic error and Random er examples.	ror with	03
	<b>(b)</b>	The output voltage of an amplifier was measured at eight intervals using the same digital voltmeter with the following 20.00, 19.80, 19.85, 20.05, 20.10, 19.90, 20.25, 19.95 V Calculate 1) Deviation of each value and 2) Standard deviate	g results:	04
	(c)	A bridge is balanced at a frequency of 1 kHz and has the freq		07

considered as a series circuit. OR Explain internal circuit diagram of Digital Frequency Meter. **07 (c)** Q.3 Give working principle, characteristics of following transducers: (a) 03 1) Thermocouple 2) Piezoelectric Which parameter we need to consider for selecting Transducers? **(b)** 04 **(c)** Explain principle of operation of LVDT in detail. **07** OR Q.3 (a) Explain function of Delay line in CRO. 03

Derive the balance condition and find the constants of arm CD,

Arm DA- R=600  $\Omega$  in parallel with C = 0.1  $\mu F.$ 

	<b>(b)</b>	Explain Ratio and Multiple Ratio measurement circuit in detail.	04
	<b>(c)</b>	Explain Lissajous method for frequency measurement in CRO.	07
<b>Q.4</b>	(a)	List out different types of attenuators used in signal Generators and	03
		explain any one in detail.	
	<b>(b)</b>	List out Digital Techniques used for Optical Isolation and explain	04
		any one in detail	
	<b>(c)</b>	Explain how Instrumentation Amplifier is used to amplify low level	07
		signal.	
		OR	
<b>Q.4</b>	(a)	Explain operation of I to P convertor in detail.	03
	<b>(b)</b>	Write a short note on variable Oscillator.	04
	<b>(c)</b>	Explain in detail how Phase difference is measure using X-OR and	07
		SR flip-flop method.	
Q.5	(a)	Draw S/H circuit using OP-AMP and explain its working in brief.	03
	<b>(b)</b>	Draw and explain Sweep Frequency Generator.	04
	<b>(c)</b>	Write a short note on Data Acquisition in PLC.	07
		OR	
<b>Q.5</b>	(a)	Draw block diagram of 1) Wave Analyzer and 2) Spectrum	03
		Analyzer.	
	<b>(b)</b>	Give difference between Single Channel DAS and Multichannel	04
		DAS.	
	<b>(c)</b>	Draw and explain working of Pulse and Square wave generator.	07

\*\*\*\*\*