Seat No.: ______

~ • •		GUJARAT TECHNOLOGICAL UNIVER BE - SEMESTER-IV(New) • EXAMINATION – WINTE	SIIY R 2016
Subj	ect	Code:2142405	Date:19/11/2016
Subj Time Instru	ect 1 e:02 ctior	Name:Analog Electronics and Its Applications :30 PM to 05:00 PM is:	Total Marks: 70
	1. 2. 3.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
			MARKS
0.1		Short Ouestions	14
C	1	Define static and dynamic resistance of the diode.	
	2	What is zener breakdown?	
	3	Define Q-Point w.r.t. transistor.	
	4	Define Noise figure of an amplifier.	
	5	Draw 1-phase full wave rectifier circuit.	
	6	Define Load Regulation w.r.t. Power supply.	
	7	What do you understand by OP-AMP?	
	8	What is utility of Active filter.	
	9	Draw the block diagram of PLL.	
	10	Define Ripple factor w.r.t. Power supply.	
	11	Enlist types of A/D converters.	
	12	Draw the OP-AMP based zero crossing detector circuit	
	13	What is a Noise immunity w.r.t. logic gate?	
	14	Enlist types of Logic families.	
Q.2	(a)	Enlist Ideal OP-AMP Characteristics.	03
-	(b)	Explain virtual ground concept w.r.t. OP-AMP. A silicon d	liode 04
		operating at a temperature of 25°C and a forward biased vol of 0.6V has a forward current of 0.8A flowing through it. Find current I_{0}	ltage d the
	(c)	Explain Summing, Scaling and Averaging Amplifier circuit necessary equation and neat sketches.	with 07
	(c)	Draw & explain Schmitt Trigger circuit with neces	ssary 07
	(0)	waveforms and equations	istar y Vi
Q.3	(a)	Calculate the values of R for 100 Hz output in a wien broscillator if C=0.001 μ F. Why it is necessary to have an ample section with a work high input impedance.	idge 03 lifier
		Section with a very high input impedance.	-1-: 0 <i>4</i>
	(D)	Plock diagram of tunical OP AMP	plain 04
	(a)	Dirive the equation of closed loop voltage gain of voltage s	orios 07
	(C)	feedback amplifier w.r.t. OP-AMP.	
0.3	(a)	Explain bootstrapping circuit with proper sketches.	03
C.C	(b)	Derive the equation of efficiency of Class-C amplifier.	04
	(c)	Draw the block diagram of a regulated DC power supply	and 07
		explain the function of each block.	
0.4	(a)	Compare DTL, TTL & RTL in tabular forms.	03
•	(b)	Explain the design of a series regulated power supply.	04
	(c)	Explain the OP-AMP based Precision Rectifier circuit.	07
		OR	

Q.4	(a)	Draw the circuit and waveform for Square wave generator using	03
		OP-AMP.	
	(b)	Explain the following terms related to the OP-AMP:	04
		(1) Input Bias current (2) SVRR (3) CMRR	
		(4) Offset voltage adjustment range	
	(c)	Explain with neat sketches F/V converter.	07
Q.5	(a)	What is Barkhausen criterion? If the feedback network of a certain oscillator provides 1% positive feedback, what should be the minimum gain for an amplifier section of the oscillator for	03
		sustained oscillation?	
	(b)	Draw sample-and-hold circuit with input and output waveforms.	04
	(c)	Define the Active and Passive Filter and Explain the OP-AMP	07
		based band Pass Filter circuit.	
		OR	
Q.5	(a)	Define Slew rate. What is the Utility of h-Parameters?	03
	(b)	Explain Switched Capacitor Filter circuit in detail.	04
	(c)	Explain the construction of AND, OR and NOT logic gates using discrete components like diode, resistor, Transistor etc.	07
