

GUJARAT TECHNOLOGICAL UNIVERSITY					
		- SEMESTER-V(New) • EXAMINATION - WINTER			
Subject C			ate:30/11/2016		
Subject N					
Time:10:	Fotal Marks: 70				
Instructions		pt all questions.			
		suitable assumptions wherever necessary.			
		s to the right indicate full marks.			
			MARKS		
Q.1		Short Questions	14		
	1	Differentiate between bipolar and unipolar devices.			
	2	Define holding current.			
	3	What is meant by rate effect?			
	4	Draw symbols of SUS and SBS.			
	5	What is valley voltage?	`		
	6	Why pulse transformer is used in firing (triggering circuit?)		
	7	Give types of commutation.			
	8	What is an ac voltage controller? Give some of it industrial applications.	S		
	9	What do you understand by harmonics?			
	10	Define conduction angle.			
	11	Enlist sources of EMI (Electromagnetic Interference).			
	12	Define line commutation.			
		What is chopper? Why it is used?			
0.2	14	State advantages of chopper drives.	0.2		
Q.2	(a) (b)	Explain Insulated Gate Commutated Thyristor (IGCT). Draw symbol and V-I characteristics of DIAC an	03 d 04		
	(b)	TRIAC.			
	(c)	Explain steady state V-I characteristics of power BJT			
		Also discuss the second breakdown phenomenon in brief OR	•		
	(c)	Explain construction of IGBT. State advantages of IGB' over power BJT.	Г 07		
Q.3	(a)	Draw and explain resistance firing circuit for SCR.	03		
Q.C	(b)	Draw and explain DIAC firing circuit.	04		
	(c)	What is snubber circuit? How elements of snubbe			
		circuits are calculated?			
		OR			
Q.3	(a)	Why gate driver circuit is required for SCR?	03		
	(b)	Explain semiconductor fuse.	04		
0.4	(c)	Describe parallel operation of thyristors.	07		
Q.4	(a)	Explain significance of freewheeling diode in controlle rectifiers.			
	(b)	Compare symmetrical semiconverter with asymmetrical semiconverter.	al 04		
	(c)	Explain operation of half wave controlled rectifier with	R 07		
	(-)	load using waveforms. Also derive expression of average			

load using waveforms. Also derive expression of average voltage for it.

Q.4	(a)	Write short note on single phase dual converter.				
	(b)	Compare half wave controlled rectifier with full wave controlled rectifier.	04			
	(c)	Draw circuit diagram of single phase fully controlled bridge converter with R-L load. Derive expression of average & RMS load voltage for it.	07			
Q.5	(a)	Explain principal of operation of chopper.	03			
	(b)	Explain working of step-down chopper with R-L load in discontinuous current mode and draw waveforms.	04			
	(c)	Explain single phase full wave converter drive in continuous conduction mode with necessary waveforms.	07			
		OR				
Q.5 (a)		Explain only four quadrant operation of dual converter.	03			
	(b)	Explain briefly principle of regenerative braking.	04			
	(c)	Explain modes of operation of current commutated chopper with its waveforms.	07			
