Seat No.: Enrolment No.
-------------------------

## GUJARAT TECHNOLOGICAL UNIVERSITY BE – SEMESTER – VI (NEW).EXAMINATION – WINTER 2016

Subject Code: 2161708 Date: 24/10/2016

**Subject Name: Power Electronics** 

Time: 10:30 AM to 01:00 PM Total Marks: 70

## **Instructions:**

1. Attempt all questions.

- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

Q.1	(a) (b)	Explain IGBT structure, Static & Dynamic Characteristics in detail. Give the difference between power MOSFET & power BJT. Explain MOSFET structure and its switching characteristics.	07 07
Q.2	(a) (b)	Write a short note on buck-boost converter.  Explain operation of six step inverter.	07 07
	(b)	Explain operation of Quasi square wave inverter with necessary waveforms.	07
Q.3	(a)	Explain working of three phase half wave controlled rectifier with load voltage waveforms at firing angle of $\alpha=0^{\circ}, \alpha=30^{\circ}$ .	07
	(b)	Explain the constructional details, working and characteristics of an SCR.  OR	07
Q.3	(a)	Explain single phase full wave bridge rectifier in detail.	07
	(b)	Write a short note on TRIAC and explain its characteristics.	07
Q.4	(a)	Explain half - controlled bridge rectifier for RL load with waveforms. What are the advantages of using flywheel diode?	07
	(b)	What is the use of snubber circuit? Explain TURN-ON snubber.  OR	07
Q.4	(a)	Explain gate drive requirement of MOSFET. Also explain any two drive circuit for it.	07
	(b)	Discuss the operation of the capacitor input filter.	07
Q.5	(a) (b)	Explain the Chopper with DC motor load with all necessary diagrams.  Explain operation of Push-Pull Converter.	07 07
<b>.</b> -		OR	07
Q.5	(a) (b)	Explain operation of half bridge inverter.  Explain Flyback Converter with necessary waveforms.	07 07

\*\*\*\*\*