## GUJARAT TECHNOLOGICAL UNIVERSITY

BE – SEMESTER V • EXAMINATION – WINTER - 2012			
Subject code: 151703 Date: 16-01-2		code: 151703 Date: 16-01-2013	
Sub	ject	Name: Electronics in Industries	
Time: 02:30 pm to 05:00 pm Total Marks: 70			
		ions:	
		Attempt all questions.	
		Make suitable assumptions wherever necessary.	
		Figures to the right indicate full marks.	
Q.1	(a)	Explain characteristics and structure of MOS Diode in detail with neat diagram	0′
	<b>(b)</b>	Explain full wave controlled bridge rectifier in detail with necessary diagrams and waveforms	0'
Q.2	(a)	With neat sketch explain structure, symbol and v-I characteristics of Silicon Controlled Switch.	0'
	<b>(b)</b>	Enlist various turn on methods of thyristor. Explain dv/dt turn on in detail. <b>OR</b>	0'
	<b>(b)</b>	Explain class C commutation technique for turning off a thyristor.	0'
Q.3	(a) (b)	Explain characteristics and structure of UJT in detail with neat sketch. Explain characteristics of MOSFET with basic operation and internal structure.	07 07
		OR	
Q.3	(a)	Explain LASCR in detail with its application.	0'
	<b>(b)</b>	Explain UJT firing circuit used to turn on thyristor in detail.	0′
Q.4	(a) (b)	Explain half wave controlled rectifier with R-L load in detail.  Explain six phase full wave controlled rectifier with its waveforms in	0' 0'
	(6)	detail.	0
		OR	
<b>Q.4</b>	(a)	Explain characteristics of TRIAC in detail with neat diagram.	0'
	<b>(b)</b>	Explain in detail snubber circuit and its use in thyristor protection.	0'
Q.5	<b>(a)</b>	Explain IGBT structure and switching characteristics in detail.	0'
	<b>(b)</b>	Explain PUT. Also explain application of PUT firing circuit for thyristor.  OR	0'
Q.5	(a)	Explain fast recovery diode in detail. How it differs from general purpose diode?	0′
	<b>(b)</b>	Explain the operation of two thyristor center tapped controlled rectifier with its input and output waveforms.	0'

\*\*\*\*\*