

GUJARAT TECHNOLOGICAL UNIVERSITY**BE – SEMESTER V • EXAMINATION – WINTER - 2012****Subject code: 152403****Date: 17-01-2013****Subject Name:****Time: 02:30 pm to 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Notations used have usual meaning.

- Q.1** (a) Discuss basic concept of power processing with neat diagram. **07**
 (b) Draw and explain peak detector circuit. **07**

- Q.2** (a) Explain log amplifier circuit using op-amp. **07**
 (b) Solve following equations using op-amp circuit. **07**

$$x + 2y - 3 = 0$$

$$2x + y - 5 = 0$$

OR

- (b) Solve the following differential equation using op-amp based circuit, **07**

$$\frac{d^2x}{dt^2} + P \frac{dx}{dt} + Qx = u$$

- Q.3** (a) Explain working of single phase controlled rectifier as a power modulator **07**
 (b) What is an active filter circuit? Discuss low pass active filter with its frequency response. **07**

OR

- Q.3** (a) Explain working of cyclo-converter circuit. Where it is used? **07**
 (b) Describe high pass active filter circuit with its frequency response. **07**

- Q.4** (a) Explain static VAR compensation in power system. **07**
 (b) Describe working of uninterrupt power supply (UPS) with its block diagram. **07**

OR

- Q.4** (a) Explain the concept and working of HVDC transmission. **07**
 (b) Discuss the inter connection of renewable energy sources and energy storage systems to the utility grid system. **07**

- Q.5** (a) Discuss in brief an application of power electronics in LED lighting. **07**
 (b) Write a brief note on followings **07**
 (1) Electroplating.
 (2) Electric welding.

OR

- Q.5** (a) Discuss working principle of DC motor drive. **07**
 (b) Explain working of precision rectifier as an analog signal processing circuit. **07**
