Seat No.:	Enrolment No.

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

## B. E. - SEMESTER – VI • EXAMINATION – WINTER 2012

Subjections: Time: Instru	ct Na 02.30 1ction 1. At 2. M	tempt any five questions. ake suitable assumptions wherever necessary.	
	3. Fig	gures to the right indicate full marks.	
Q.1	(a)	Explain the following terms.  1. A course of 2. Precision 2. Precision 4. Sensitivity.	07
	<b>(b)</b>	1. Accuracy 2. Precision 3. Resolution 4. Sensitivity Explain Maxwell's Bridge for measurement of self-inductance.	07
Q.2	(a)	Usages of Wein's Bridge and derive the expression of frequency in terms of its parameters.	07
	<b>(b)</b>	Usages of De Sauty's Bridge and derive the equation for the same.  OR	07
	<b>(b)</b>	Derive the equation of capacitance and dissipation factor according to the working of Schering Bridge.	07
Q.3	(a) (b)	Principle and working of Digital LCR meter Kelvin's double bridge, explain its working with diagram.  OR	07 07
Q.3	(a) (b)	Explain Anderson's Bridge.  Measurement of earth resistance, describe methods with diagram.	07 07
Q.4	(a) (b)	Describe the Varley loop test.  Explain construction and working of flux meter.  OR	07 07
Q.4	(a)	Derive equation for ratio and phase angel error of a potential transformer.	07
	<b>(b)</b>	What are the problems with measurement of high resistance? Derive equation for measurement of insulation resistance.	07
Q.5	(a) (b)	Explain Heterodyne wave analyzer with necessary block dia.  Explain construction and working of current transformer.  OR	07 07
Q.5	(a)	Which methods are used for measurement of low resistance, explain	07
	<b>(b)</b>	any one.  Describe the method for determination of B-H curve of magnetic material.	07