

GUJARAT TECHNOLOGICAL UNIVERSITY**B. E. - SEMESTER – VI • EXAMINATION – WINTER 2012****Subject code: 162003****Date: 04/01/2013****Subject Name: Control of Electric Drives****Time: 02.30 pm - 05.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a)** Explain the generalized block diagram of Electric Drive and state advantage of it. **07**
(b) Explain the Four quadrant operation of Electrical Drive. **07**
- Q.2 (a)** Explain the output voltage, output current, source current and thyristor current waveforms for type-C chopper for its operation in second quadrant. **07**
(b) A motor drives two loads. One has rotational motion. It is coupled to the motor through a reduction gear with $a=0.1$ and efficiency of 90%. The load has a moment of inertia of 10 kg-m^2 and a torque of 10 N-m . Other load has translational motion and consists of 1000 kg weight to be lifted up at an uniform speed of 1.5 m/s . Coupling between this load and the motor has an efficiency of 85%. Motor has an inertia of 0.2 kg-m^2 and runs at a constant speed of 1420 rpm . Determine equivalent inertia referred to the motor shaft and power developed by the motor. **07**
- OR**
- Q.3 (b)** Explain the field control of DC shunt motor in details. **07**
Q.3 (a) Describe the principle of step-up choppers. Derive an expression for the average output voltage in terms of input voltage and duty cycle. State the assumption made. **07**
(b) Explain the Four quadrant Operation of Chopper circuit **07**
- OR**
- Q.3 (a)** Derive the Steady state Time Domain analysis of Type-A chopper and derive the maximum and minimum value of load current **07**
(b) A step up chopper has input voltage of 220 V and output voltage of 660 V . If the conducting time of thyristor chopper is $100 \mu\text{s}$, compute the pulse width of output voltage. In case output voltage pulse width is halved for constant frequency operation, find the average value of new output voltage. **07**
- Q.4 (a)** Explain Single phase Half wave uncontrolled rectifier Circuit with RL load and draw necessary waveform with performance parameter. **07**
(b) Explain the single phase fully controlled bridge converter with R-L-E load draw the necessary waveform with conduction table. **07**
- OR**
- Q.4 (a)** Explain the operation and Analysis of Three phase uncontrolled rectifier with R-L load with necessary waveform and conduction table. **07**
Q.4 (b) Explain Single phase half wave controlled rectifier circuit with purely resistive load and also derive the performance parameter. **07**
- Q.5 (a)** Describe the operation of a single stack variable reluctance stepper motor. **07**
(b) Explain the methods for controlling the single phase ac induction motor with diagram. **07**
- OR**
- Q.5 (a)** Explain the methods for controlling the universal motor. **07**
(b) Derive the Equivalent values of Drive parameters with Rotational load. **07**