04

07

GUJARAT TECHNOLOGICAL UNIVERSITY B. E. - SEMESTER – VI • EXAMINATION – WINTER 2012


| Subject code: 162405 | Date: 07/01/2013 | |
|--|------------------|--|
| Subject Name: Power Processing Circuit - I | | |
| Time: 02.30 pm - 05.00 pm | Total Marks: 70 | |
| Instructions: | | |
| 1. Attempt any five questions. | | |

- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- 4. Notations /symbols used have usual meaning.

Q.1 (a) Classify the rectifiers in detail.

- (b) Justify the statement "Free wheeling diode improves the power 03 factor of a system".
- (c) Derive an expression for the (i) average load voltage (ii) RMS 07 load voltage and (iii) average load current; for the single phase controlled rectifier with inductive load.
- Q.2 (a) Describe the control strategies used for Chopper. 07
 - (b) Explain with neat power diagram and associated waveforms 07 the operation of three- phase uncontrolled rectifier with resistive load.

OR

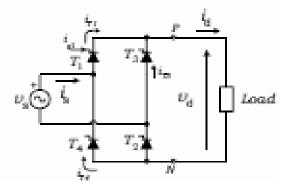

For the above circuit assume inductive –resistive load and draw all associated waveforms. State the name of the above circuit.

- Q.3 (a) Enlist three terminals IC based linear regulators and explain 07 any one in detail.
 - (b) Describe operating principle of SEPIC converter. 07

OR

- Q.3 (a) Why power supply is needed? Explain voltage mode control 07 of power supply with schematic diagram and waveform.
 - (b) Analyze the performance of the boost converter with 07 continuous load current .Also, draw the relevant waveforms.
- Q.4 (a) Describe the voltage commuted chopper with necessary voltage 08 and current waveforms as a function of time.

| | (b) | Discuss the working principle of Cuk converter. | 06 |
|-----|-------------|---|-----------|
| | | OR | |
| Q.4 | (a) | Draw and explain the Jone's chopper circuit in detail. Enlist its application(s). | 08 |
| Q.4 | (b) | Discuss the working principle of Full- bridge converter. | 06 |
| Q.5 | (a) | Write a technical note on: ZCS. | 06 |
| | (b) | Explain modeling of an isolated dc-dc converter circuit. OR | 08 |
| Q.5 | (a) | Write a detailed note on: Resonant switch converter. | 06 |
| | (b) | Compare (I) Half controlled –Full controlled rectifier. (II) Fly back – Forward converter. | 08 |
