Sea	at No.: Enrolment No	
	GUJARAT TECHNOLOGICAL UNIVERSITY	
a ·	B. E SEMESTER – VII • EXAMINATION – WINTER 2012	
	bject code: 172403 Date: 01/01/2013	
	bject Name: Power Processing Circuits - II	
	me: 10.30 am - 01.00 pm Total Marks: 70	
Ins	structions:	
	 Attempt any five questions. Make suitable assumptions wherever necessary. 	
	3. Figures to the right indicate full marks.	
(a)	Define Inverter and draw only the power schematic of a three phase full bridge inverter. Also list and explain the performance parameters of it.	07
(b)	List different types of PWM used for the control of inverters. Explain trapezoidal and sine triangle PWM with neat diagrams.	07
(a)	6	07
(b)	Dwell Time, Modulation Index, Cyclo-converter, UPS, THD, MTTR, MTBF.	07
(b)	Draw and explain L-Type ZCS resonant inverter with neat waveforms. OR	U/
(b)	Explain 180 degree conduction mode of inverter with line and phase voltage waveforms. State the equations for line and phase voltage.	07
(a)	Classify multilevel inverters. Explain the basic principle of multilevel inverter giving its applications.	07
(b)	Draw the schematic diagram of a UPS indicating all the necessary parts. List the four main parts of an UPS and describe each in brief with neat diagram.	07
, .	OR	
(a)	A 20 KVA UPS is to be employed for RL load with power factor of 0.8. The backup time required is 30 minutes. Assuming the UPS efficiency to be 85%, select a suitable Pb-Acid battery (find KW/cell capacity) for the same. Take minimum allowable battery	07

Q.1

Q.2

Q.3

Q.3

voltage as 24 Volts and final V/cell=1.75 V.

(b) List the different types of batteries & explain the battery charging process in detail.

Q.4 (a) Explain Modified Mc-Murray Bedford Full-bridge inverter with necessary circuit and 07 waveforms.

(b) Differentiate between a static switch and an electro-mechanical switch. Explain the **07** working of a 3-phase static switch with neat diagram.

OR

Q.4 (a) Explain the working of a full bridge square wave inverter with circuit diagram and 07 waveforms.

Q.4 (b) Explain Integral Cycle Control method for AC voltage controllers. 07

Q.5 (a) Explain the Fourier analysis of a square wave inverter and thus derive the THD in the 07 output voltage waveform.

(b) Describe in detail, the working principle of an Active Front-end rectifier with necessary 67 figures.

OR

Q.5 (a) Explain the input side control techniques of an inverter with necessary diagrams.

(b) State the main drawbacks of controlled rectifiers and justify the use of Active Front-end or rectifiers giving applications and advantages.
