GUJARAT TECHNOLOGICAL UNIVERSITY B.E. - SEMESTER – VIII EXAMINATION – OCTOBER 2012

Subject Code: 182401Date: 27/10/2012Subject Name: Power Electronics Applications in Power SystemTime: 02.30pm - 05.00pmTotal Marks: 70

Instructions:

- 1. Attempt any five questions.
- 2. Make suitable assumptions wherever necessary.
- **3.** Figures to the right indicate full marks.
- 4. Notations used have usual meaning.
- Q.1 (a) Discuss the problems with AC transmission. How HVDC transmission can be 07 compared with AC transmission.
 - (b) Discuss the Factors limiting loading capability of transmission line. 07
- Q.2 (a) Write brief note on wind and small hydro connection.
 - (b) Two six pulse converters, used for bipolar HVDC transmission system, are 07 rated 1000 MW, ± 200 kV. Calculate the rms current and peak reverse voltage ratings for each of the thyristor.

OR

(b) In bipolar HVDC system, converter is supplied through 3 phase, 11000 V, 50 07 Hz ac supply system. The input transformer has leakage inductance of 10 mH per phase. The current in dc line is 300A. For firing angle of 15°, calculate its output voltage and DC link voltage.

Q.3 (a) Explain TCR flexible transmission controller with neat diagram. 07

(b) Write brief note on standards related to power quality in power system. 07

OR

- Q.3 (a) Discuss the concept of phase angle compensation in flexible AC transmission. 07
 - (b) Explain Unified Power Flow Controller (UPFC) for flexible AC transmission. 07
- Q.4 (a) Discuss bipolar link in HVDC system with merits and demerits.
 (b) Explain interconnection of Renewable Energy Source to utility grid.
 OR
 Q.4 (a) Describe interface for a bidirectional power flow with neat diagram.
 Q.4 (b) Discuss converter characteristics used in HVDC system.
 O7
- Q.5(a) Explain basic twelve pulse converter used in high voltage DC system.07(b) Discuss the need for improved utility interface in AC transmission..07

OR

Q.5 (a) Explain directional static over current relay with neat block diagram.
 (b) Discuss basic principle of differential relay? Draw and Explain block diagram
 07
 07
 07

1

07