

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-IV • EXAMINATION – WINTER 2013****Subject Code: 142402****Date: 30-12-2013****Subject Name: Fundamentals of Power Electronics****Time: 02:30 pm to 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Draw and explain block diagram of Power Electronics System. **05**
 (b) Fill in Blanks. **03**
 (1) _____ works as a relaxation oscillator.
 (2) Diode that can works on a.c. is called _____
 (3) _____ Operate at very low voltage.
- (c) Define Commutation Explain Class-A Commutation with necessary waveforms. **06**
- Q.2** (a) Write a detailed note on Turn- on Methods of SCR. **07**
 (b) Define DIAC. Draw and explain schematic construction, symbol and V-I characteristic of DIAC. **07**
- OR**
- (b) Draw structure, symbol and Equivalent circuit of UJT. Also derive equation for periodic time T of UJT relaxation oscillator. **07**
- Q.3** (a) Explain 1-phase Cycloconverter in detail. **07**
 (b) Draw and explain single phase MC-MURRAY Inverter circuit with suitable waveforms. **07**
- OR**
- Q.3** (a) Write a detailed note on AC Chopper. **07**
 (b) Classify Inverter. Explain basic series Inverter with voltage and current waveforms. **07**
- Q.4** (a) Draw and explain STEP-UP Chopper with necessary equation. **07**
 (b) Define TRIAC. Enlist all triggering modes of TRIAC and explain the most sensitive mode. **07**
- OR**
- Q.4** (a) Enlist and explain control strategies employed in d.c. choppers. **07**
 (b) Draw and explain schematic construction, symbol and V-I characteristic of LASCR. **07**
- Q.5** (a) Explain dv/dt and di/dt protection of SCR. **07**
 (b) Compare half controlled and full-controlled rectifiers. **07**
- OR**
- Q.5** (a) Make a comparison chart of power semiconductor devices. **07**
 (b) Explain with the help of neat power diagram and associated waveforms, the operation of 1-phase half-wave controlled converter with Resistive and Inductive load. **07**
