Seat No.:	Enrolment No
-----------	--------------

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-V • EXAMINATION - WINTER 2013

Subject Code: 151003 Date: 29-11-2013 **Subject Name: Integrated Circuits and Applications** Time: 10.30 am - 01.00 pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. 0.1 (a) What information is contained in a typical op-amp datasheet? Briefly explain. 07 List three basic temperature grades for IC. What is the temperature range of 741C and 741A op-amp? (b) Which type of feedback Non-inverting op-amp has? Derive input impedance **07** and bandwidth with feedback for it. Draw the circuit diagram. **Q.2** A 741 op-amp as inverting amplifier is driven by peak to peak 10 volt sine 04 (a) (i) wave. The closed loop gain is 4. Supply voltage of op-amp is +/-15V.Draw input and out waveforms. Show values of output peak voltage also. Give your remarks about output. (ii) Define PSRR of an op-amp. In an op-amp PSRR is $150\mu V/V$. If supply 03 voltage is changed from +10V to +12V, What is the change in input offset voltage V_{io}? (b) Draw the differential amplifier circuit using single op-amp and derive the **07** expression for output voltage as a function of input voltages. Comment on its input resistance. (b) Consider an inverting operational amplifier with $R_F=100K\Omega$ and $R_1=1K\Omega$. 07 Input offset voltage drift is 30µV/°C and input offset current drift is 300Pa/°C. Assume the amplifier is nulled at 25°C. Calculate the value of error voltage E_v and output voltage at 35°C if V_{in}=1mV dc. (a) Explain voltage to current converter with floating load. Based on that show low **07** 0.3 voltagedc voltmeter circuit and discuss it. (b) What do you understand by precision rectifier? Draw half wave precision 07 rectifier circuit and explain with necessary waveforms. OR 0.3 (a) Draw and explain summing amplifier circuit using op-amp in inverting **07** configuration based on that design a circuit such that $V_0 = -2(3V_1 + 4V_2 + 2V_3)$. (b) Explain op-amp based inverting comparator circuits with (i) positive reference 07 voltage (ii) negative reference voltage. Show necessary waveforms. (a) Draw the internal block diagram of 555 timer IC and explain the operation in **07 Q.4** monostable mode. 07 Explain op-amp based positive clipper circuit with necessary waveforms. Draw **(b)** output waveforms for (i) Positive reference voltage (ii) Negative reference voltage. Assume input signal is sine wave. Explain how op-amp can be used to generate free running square wave with 0.4 07 necessary circuit diagram and waveforms. Show how time period can be calculated. (b) Explain the operation of 555 IC based a stable multivibrator with necessary 07

circuit diagram and waveforms.

Q.5	(a)	Classify filters with four basic types. Explain ideal and practical characteristics	07
	(b)	of all. Draw attenuation characteristics also.	07
	(b)	Discuss fixed voltage regulators and adjustable voltage regulator with necessary circuit diagrams.	U/
		OR	
Q.5	(a)	Explain magnitude and phase response of low pass function for biquad circuit.	07
	(b)	Explain the operating principle of Phase Locked Loop	07
