GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-V • EXAMINATION - WINTER 2013

Subject Name: Applied Power Electronics Date: 04-12-201		,	
Tir	•	0.30 am - 01.00 pm Total Marks: 70	
	2. 3.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. Notations used have usual meaning.	
Q.1	(a) (b)	Discuss concept of power processing with neat block diagram. Explain working of anti-log amplifier circuit.	07 07
Q.2	(a)	Explain working of peak detector circuit with neat diagram. Draw relevant waveforms.	07
	(b)	Discuss the concept of switch capacitor circuit. Also draw inverting and non-inverting amplifier circuit based on switch capacitor circuit. OR	07
	(b)	Explain low pass filter circuit. Draw its frequency response.	07
Q.3	(a) (b)	Draw and explain DC-DC power converter as a basic power modulator. Explain op-amp based high pass filter circuit. Also draw its response. OR	07 07
Q.3	(a) (b)	Explain state variable filter circuit with illustration. Discuss concept of HVDC transmission. Also compare it with AC transmission.	07 07
Q.4	(a) (b)	Explain switch mode power supply (SMPS) with neat diagram. Draw a block diagram of PLL and explain working of each block. OR	07 07
Q.4	(a) (b)	Explain basic working of AC-DC controlled rectifier circuit. Draw and explain charging circuit for battery.	07 07
Q.5	(a) (b)	Write a brief note on static VAR compensation. Discuss working of DC drive system with block diagram. OR	07 07
Q.5	(a)	Write a short note on followings, (1) Induction heating. (2) Electric welding.	07
	(b)	Discuss LED lighting as a consumer electronics application.	07
