## **GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-VI-. EXAMINATION – WINTER 2013**

•			Date: 27/11/2013	
Subject Name: Integrated Circuit & Application Time: 2:30pm To 5:00pm Instructions:			Total Marks: 70	
	2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a)	Define Op-Amp. Draw and explain block diagram representation of a typical Op-Amp.	07	
	<b>(b)</b>	*1 1	07	
Q.2	(a) (b)	For a non-inverting amplifier, the values of $R_1$ and $R_f$ are $1k\Omega$ and $10k\Omega$ respectively. The various op-amp parameters are, Open loop gain = $2 \times 10^5$ , Input Resistance = $2 M\Omega$ , Supply voltages = $\pm 12 V$ , Output Resistance = $75 \Omega$ , Single break frequency = $5 Hz$ Calculate closed loop gain, input resistance, output resistance and bandwidth with feedback.	07 07	
	<b>(b)</b>	For the practical inverting amplifier, the values of $R_1$ and $R_f$ are $470\Omega$ and $4.7k\Omega$ . The various op-amp parameters are, Open loop gain = $2 \times 10^5$ , input resistance = $2M\Omega$ , Supply voltages = $\pm$ 15 V, Output resistance = $75\Omega$ , single break frequency = $5$ Hz Calculate the closed loop voltage gain, input resistance, output resistance and bandwidth with feedback.	07	
Q.3	(a) (b)		07 07	
Q.3	(a) (b)	Explain V-I converter with (i) Floating Load, (ii) Grounded Load.	07 07	
Q.4	(a) (b)	Write short note on Negative Clipper circuit.  Explain the operation of Sample & Hold circuit with its applications.  OR	07 07	
Q.4	(a) (b)	Explain precision Full Wave Rectifier in detail. Write short note on Basic Log Amplifier using diode.	07 07	
Q.5	(a) (b)	Explain Monostable Multivibrator as a frequency divider and pulse width Modulator in detail.	07 07	
Q.5	(a)		07	
	<b>(b)</b>	demodulator.  Explain block diagram and operation of Phase Locked Loop.	07	

\*\*\*\*\*

**70**