GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-VI • EXAMINATION - WINTER 2013

Subject Code: 160902

Date: 29-11-2013

Subject Name: Power Electronics-II Time: 02:30 pm to 05:00 pm **Instructions:**

Total Marks: 70

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 Draw the power circuit of a parallel inverter and discuss its operation. Also explain how voltage 07 (a) control can be obtained with this inverter.
 - (b) List the commonly used PWM technique for voltage waveform and control of inverter. Explain 07 any one in details.
- Describe using a neat circuit diagram, waveform and operation of PWM inverter and also 07 Q.2 (a) explain how the output voltage can be controlled in this scheme.
 - (b) Explain the operation of a single phase voltage controller supplying R-L load when the firing 07 angle " α " is

(1) less than the load angle Φ (2) equal to load angle Φ (3) greater than load angle Φ .

OR

- (b) Write a brief note on 1 phase AC voltage controller with PWM control with necessary 07 waveforms.
- A three phase bridge inverter has 180° conduction interval for it's SCRs. Draw it's power Q.3 (a) 07 circuit and state the conduction sequences of the SCRs with necessary waveforms.
 - Draw the torque speed characteristics of 3 phase Induction motor and explain the following (b) 07 regions. (1).Plugging (2).Motoring (3).Generating.

OR

- Q.3 (a) Distinguish VSI and CSI and specify their applications. 07
 - Classify the various control strategies for speed control of 3 phase induction motor. Explain the 07 (b) operation of a constant V/F control for the Induction motor with neat schematic diagram.
- Q.4 Describe the principle of working of a single phase to single phase bridge type step down 07 (a) cycloconverter feeding R-L load.
 - Describe in brief matrix converter. (b)

OR

07

Q.4 Distinguish circulating current mode and non circulating current mode with cyclo converter. 07 (a)

- (b) State the various points of comparisons and their choice/criterion for selection between AC and 07 DC drives.
- Q.5 Explain the operation of a self controlled (closed loop) synchronous motor drive fed from a 07 (a) load commutated inverter to control the speed of synchronous motor with necessary schematic diagram.
 - Draw the neat circuit diagram and explain the speed control of 3 Ø Induction motor by static 07 (b) Scherbius system.

OR

- State the advantages of HVDC over conventional AC transmission system. Draw the schematic Q.5 07 (a) diagram of basic HVDC transmission system and explain in brief.
 - 07 Draw the circuit for a static DC circuit breaker and discuss its advantages and disadvantages. (b)
