

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VI • EXAMINATION – WINTER 2013****Subject Code: 162404****Date: 06-12-2013****Subject Name: Industrial Drives and Control-I****Time: 02:30 pm to 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Notations used have usual meaning.

- Q.1** (a) Draw block diagram of DC drive system and explain it. **07**
(b) Explain speed control of separately excited DC motor with field control method. Discuss its application. **07**
- Q.2** (a) Discuss the working of single phase semi-converter with R-L load. Draw appropriate wave forms. **07**
(b) The DC series motor of 20 h.p., 220V, and 1000 rpm is controlled by a single phase semi-converter. The combined field and armature circuit resistance is 0.2 ohm. Assume Motor constant is $K=0.03 \text{ N-m/Amp}^2$ and ripple free motor current. The converter is supplied with 250 Vac. Determine the (1) motor current (2) motor torque at rated speed for a firing angle of 30° . **07**
- OR**
- (b) Obtain an expression for output voltage and current of the boost chopper circuit. **07**
- Q.3** (a) Explain operation of DC motor in two quadrants with phase controlled converter. **07**
(b) Discuss closed loop operation of DC motor with current limit control. **07**
- OR**
- Q.3** (a) Explain class A chopper circuit for DC motor control. Draw relevant waveforms. **07**
(b) Compare control of DC motor based on phase control converter and chopper. **07**
- Q.4** (a) Explain PI controller with suitable example. **07**
(b) Discuss half wave controlled converter with relevant waveforms. **07**
- OR**
- Q.4** (a) Explain chopper based implementation of braking for DC motor. **07**
(b) Write a brief note on selection of motor power rating with illustration. **07**
- Q.5** (a) Write a brief note on constant torque and constant horse power operation of DC motor. **07**
(b) Explain multi-phase chopper circuit with waveforms. **07**
- OR**
- Q.5** (a) Explain control of DC motor with phase locked loop. **07**
(b) Discuss the permanent magnet motor drive. **07**
