| Seat No.: | Enrolment No. |
|-----------|---------------|
|           |               |

## GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-VII • EXAMINATION - WINTER 2013

DE - SEMESTER-VII - EXAMINATION - WINTER 2013

| Subject Code: 170906 |                  |   | Date: 03-12-2013 |  |
|----------------------|------------------|---|------------------|--|
| •                    | e: 10:<br>ctions | ame: Advanced Power Electronics-I 30 TO 01:00 Total Marks:  Attempt all questions.  | 70               |  |
|                      | <b>2.</b> I      | Make suitable assumptions wherever necessary.<br>Figures to the right indicate full marks.  |                  |  |
| Q.1                  | (a)<br>(b)       | Explain two quadrant ZVS converter.<br>Compare multilevel inverter with 2-level inverter. Explain flying capacitor based 3-level inverter with neat sketch. | 07<br>07         |  |
| Q.2                  | (a)              | What is difference between isolated and non isolated dc power supply. Explain fly back converter topology with diagram and wave forms.                      | 07               |  |
|                      | <b>(b)</b>       | Discuss working principle of parallel inverter. Give its application area.  OR  | 07               |  |
|                      | <b>(b)</b>       | Explain operation of ZCS converter with diagram and wave forms.   | 07               |  |
| Q.3                  | (a)              | Discuss operation of cascaded H-bridge multilevel inverter. Give its merits and limitations.  | 07               |  |
|                      | <b>(b)</b>       | Discuss components of UPS.  | 07               |  |
| Q.3                  | (a)              | <b>OR</b> Discuss operation of diode clamped multilevel inverter. Discuss its merits and limitations.   | 07               |  |
|                      | <b>(b)</b>       | Explain working of forward converter with diagram and wave forms.   | 07               |  |
| Q.4                  | (a)              | Explain transformer connections of 18-pulse converters. Compare it with 6-pulse converter.  | 07               |  |
|                      | <b>(b)</b>       | Explain difference in sinusoidal and trapezoidal BLDC machine.  OR  | 07               |  |
| Q.4                  | (a)<br>(b)       | Compare multi-pulse converter with multi-level inverter. Discuss current control of BLDC drive.   | 07<br>07         |  |
| Q.5                  | (a)<br>(b)       | Discuss working principle of SRM. Explain block diagram of SRM drive. Give classification of stepper motor. Discuss stepper motor drive.  OR                | 07<br>07         |  |
| Q.5                  | (a)<br>(b)       | Discuss difference between on line and off line UPS. Discuss torque-angle characteristics of stepper motor.   | 07<br>07         |  |

\*\*\*\*\*