Seat No.:	

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

## BE - SEMESTER-VII • EXAMINATION – WINTER 2013

•	•	Code: 172403 Date: 07-12-2013	
•	e: 10	Name: Power Processing Circuits-II 0:30 TO 01:00 Total Marks: 70	
	1.	Attempt all questions.  Make suitable assumptions wherever necessary.  Figures to the right indicate full marks.	
Q.1	(a)	Describe the operation of a three phase bridge inverter for 180° conduction for star connected resistive load	10
	<b>(b)</b>	Differentiate: On-line and Off-line UPS.	04
Q.2	(a) (b)	Why Inverter is used? Give detailed classification of inverter. Enlist its area(s) of application(s) where inverter is suitable.  Analyse performance of the circuit shown in Fig.1	07
		$ \begin{array}{c c} \hline  & \downarrow & \downarrow & \downarrow \\ \hline  & \downarrow & \downarrow & $	
	<b>(b)</b>	<b>OR</b> With waveforms, explain the operation of a 1-Ø to 1-Ø cyclo-converter.	07
Q.3	(a) (b)	Explain working principle of a single – phase series inverter.  Why multi-level inverter is required? Discuss one application of the same.  OR	07 07
Q.3	(a) (b)	Describe operation of a single – phase full bridge inverter.  Explain diode clamped multi-level inverter.	07 07
Q.4	(a) (b)	Enlist DC input voltage control techniques for inverter. Explain any one of them. Write short note on: McMurray Inverter.  OR	07 07
Q.4	(a) (b)	State various types of PWM techniques & describe any one of them in detail. Write short note on: SVPWM.	07 07
Q.5	(a)	Why battery is required? Explain constant current and trickle charging methods for battery.	04
	<b>(b)</b>	Write short note on: - Active front-end rectifier.  OR	10
Q.5	(a)	With help of block diagram explain the basic principle of operation of a on-line UPS.	04
	<b>(b)</b>	State disadvantages of controlled rectifier. Justify the use of Active front-end rectifier.  ***********************************	10