

GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-III • EXAMINATION – WINTER • 2014

Subject Code: 130901Date: 01-01-2015Subject Name: Circuits and Networks			
Tim	Total Marks: 70		
Instr	1. 2.	ns: Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a) (b)	Explain the terms (i) Linear (ii) Bilateral (iii) Passive (iv) Reciprocal (v) Time invariant (vi) Lumped parameter and (vii) Dual with reference to Network. Derive formulae to convert given 'Y' parameters into 'h' parameters.	07 07
Q.2	(a) (b)	Calculate VX in the circuit of Figure 1 using (a) nodal analysis and (b) Superposition. Describe Laplace transformation method for solving differential equations; state its advantage over the classical method.	04 03 07
	(b)	OR (i) Derive Laplace transform of derivatives and integrals. (ii) Find Laplace transform of sinωt.	07
Q.3	(a) (b)	Explain incident matrix of a linear oriented graph with example. State and explain (i) Reciprocity theorm (ii)Nortons Theorm. OR	07 07
Q.3	(a) (b)	The incidence matrix of a graph is as shown in Fig 2 Obtain the corresponding graph. Prepare the circuit graph, graph tree and hence cut set matrix for circuit shown in figure 3.	07 07
Q.4	(a) (b)	Using Nodal Analysis find Vo in the circuit of figure 4 Find Vo in the circuit of figure 5 using principle of superposition. OR	07 07
Q.4	(a) (b)	Using loop Analysis find Vo in the circuit of figure 6. Determine the impedance seen by the source in the circuit in Fig 7.	07 07
Q.5		Use the differential equation approach to find $i(t)$ for $t > 0$ in the circuit in Fig. 8 and plot the response including the time interval just prior to opening the switch	07
	(b)	Explain the dual network and concept of duality with suitable Example. OR	07
Q.5	(a) (b)	Discuss concept of poles and zeros in a network function. Discuss substitution theorem and steps for solution of a network using this theorem.	07 07

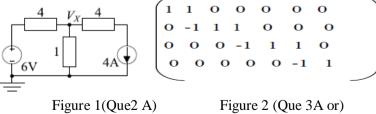

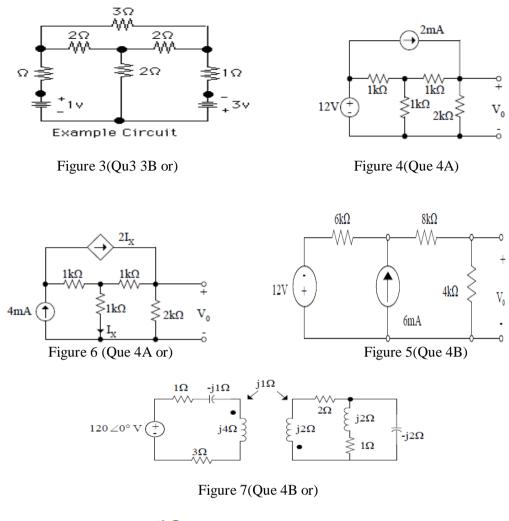

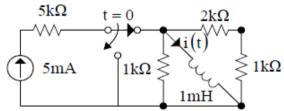


Figure 8(Que 5 A)
