GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-III • EXAMINATION – WINTER • 2014

	Subject Code: 130902Date: 23-12-2014Subject Name: Analog and Digital ElectronicsTotal Marks: 70Time: 02.30 pm - 05.00 pmTotal Marks: 70Instructions:Total Marks: 70			
Ti				
Ins	1. 2.	Attempt all questions.		
Q.1	(a)	What are ideal characteristics of operational amplifier?	07	
	(b)	Explain block diagram of op-amp. Explain function of each block.	07	
Q.2	(a)	Explain inverting, noninverting and differential amplifier using op-amp under open loop condition.	07	
	(b)	Derive equation of gain for voltage series feed-back for op-amp. OR	07	
	(b)	Draw pin diagram of op-amp. Explain function of each pin. Explain different packages are used for op-amp IC.	07	
Q.3	(a) (b)	Explain application of op-amp as integrator and differentiator. What is the importance of slew rate and output offset voltage in operation of op- amp?	07 07	
• •		OR	~-	
Q.3	(a)	What are demerits of open loop configuration of op-amp? How can we overcome this?	07	
	(b)	Explain differential amplifier using three op-amp. Derive its gain equitation.	07	
Q.4	(a)	Why NAND gate and NOR gate is known as universal gate? Obtain AND and OR gate using NAND and NOR gate.	07	
	(b)	Explain working of IC 555 as astable multivibrator. OR	07	
Q.4	(a) (b)	Explain pin diagram of IC 555. Explain function of each pin. Explain half adder and full adder circuit.	07 07	
Q.5	(a) (b)	Explain R-S flip-flop using truth table. Explain role of multiplexer and demultiplexer in digital electronics. Explain with diagram.	07 07	
Q.5	(a)	OR How can be obtained 1's and 2's compliment of binary number?	07	
Q. 3	(a) (b)	Explain working of counter and register.	07 07	
