GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-IV • EXAMINATION – WINTER • 2014

| Subject Code: 142402 Date: 02-01-2015 | | | |
|--|----------------|---|----------|
| Subject Name: Fundamentals of Power Electronics | | | |
| Time: 02:30 pm - 05:00 pm Total Marks: 70 Instructions: | | | |
| | 1. 2. 3. | Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. | |
| Q.1 | (a) | Define Power Electronics. Draw detailed static Anode-Cathode characteristic of a thyristor and Explain it. | 07 |
| | (b) | Draw & Explain the schematic diagram, symbol and V-I characteristic of LASCR. | 07 |
| Q.2 | (a) | Write a detail note on:- TURN ON methods of SCR. | 07 |
| | (b) | Describe the construction and working of SCR using two transistors Analogy. OR | 07 |
| | (b) | Explain UJT characteristics. How UJT works as relaxation oscillator? | 07 |
| Q.3 | (a) | Define DIAC. Draw & Explain schematic diagram, symbol and V-I characteristic of DIAC. | 07 |
| | (b) | Draw & Explain equivalent circuit and transient response of Fast Recovery diode. | 07 |
| 0.2 | (-) | OR | 07 |
| Q.3 | (a) (b) | Enlist all triggering modes of TRIAC. Explain most sensitive mode. Draw Schematic diagram and symbol of IGBT. Explain in detail the operation of IGBT. | 07 07 |
| Q.4 | (a) | Explain dv/dt and di/dt protection of SCR. | 07 |
| - | (b) | What do you mean by cycloconverter? Explain 1-phase cycloconverter in detail. OR | 07 |
| Q.4 | (a) | Compare 1-phase & 3-phase uncontrolled rectifier. | 07 |
| | (b) | Write a detailed note on: - Power switch classification. | 07 |
| Q.5 | (a) | Define Chopper. Enlist and Explain the control strategies employed in DC chopper for operating the switches. | 07 |
| | (b) | Define & Classify Invertes. Draw & Explain the schematic diagram of basic series inverter. | 07 |
| 05 | (z) | OR | 07 |
| Q.5 | (a) | Explain Principles of operation of STEP-UP/DOWN Chopper and derive equation for output voltage. | 07 |
| | (b) | Draw & Explain single phase MC-MURRAY Inverter circuit with voltage and current waveforms. | 07 |
