Seat No.:	Enrolment No.
Jean NO.	Enrollneni No

Subject Code: 152401

GUJARAT TECHNOLOGICAL UNIVERSITY

Date: 26-11-2014

BE - SEMESTER-V • EXAMINATION - WINTER • 2014

Sub	ject	Name: Power Electronics Devices and Components	
Time: 10.30 am - 01.00 pm Total Marks: 70			
	uction	▲	
	1.	Attempt all questions.	
		Make suitable assumptions wherever necessary.	
	3.	Figures to the right indicate full marks.	
	4.	Notations/ symbols used have usual meanings.	
Q.1	(a)	Compare for various aspects in tabular form.	08
V.1	(4)	(i) Rectifier diode with Power diode	00
		(ii) Converter grade thyristor with inverter grade thyristor.	
	(b)	Discuss switch specifications in detail.	06
	` '		
Q.2	(a)	Explain cooling, heat sink and mounting requirements for a power device.	07
	(b)	Derive an equation for oscillating frequency for an UJT relaxation oscillator.	07
		OR	
	(b)	Explain (i) pulse transformer (ii) Opto-coupler.	07
Q.3	(a)	Enlist various power diodes. State its applications. Describe the principle of operation	07
		of a power diode.	
	(b)	Discuss the switching characteristic of a Power BJT with relevant waveforms. OR	07
Q.3	(a)	Discuss working of a Power Darlington circuit.	07
	(b)	Describe reverse recovery characteristics of a diode with necessary diagram(s).	07
Q.4	(a)	Describe Turn-on mechanism for a Thyristor with necessary waveforms.	07
	(b)	Draw and explain two transistor model of an SCR.	07
	. ,	OR	
Q.4	(a)	State requirements for successful commutation. Explain Class A commutation method for thyristor.	07
	(b)	List thyristor protections required for reliable operation. Discuss any two of them in	07
	(D)	detail.	U/
Q.5	(a)	Discuss switching characteristic of IGBT.	07
	(b)	Write notes on :- TRIAC	07
	` '	OR	
Q.5	(a)	Write notes on :- GTO	07
	(b)	Sketch symbol and equivalent circuit of depletion type Power MOSFET. Describe its	07
		operation.	
