# **GUJARAT TECHNOLOGICAL UNIVERSITY** BE - SEMESTER-V • EXAMINATION – WINTER • 2014

Subject Code: 152405

#### Subject Couce. 132403 Subject Name: Power Electronics Applications

# Date: 08-12-2014

Time: 10.30 am - 01.00 pm

# **Total Marks: 70**

## Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Draw the block diagram of power electronics system & explain functionality & 07 working of each in detail.
  - (b) Do as directed: 1.Draw the detail block diagram indicating all parts of electric 07 motor drive. 2. Enlist the function of power electronics modulator in drive system. 3. List the advantage & disadvantages of electrical drive.
- Q.2 (a) What is thyrister! Explain its construction, operating principle & v-I charact. Of 07 S.C.R.
  - (b) Draw symbols &v-I charact. Of 1.power diode 2.D.I.A.C.3.POWER 07 B.J.T.4.U.J.T.5.TRAC 6.POWER MOSFET 7.I.G.B.T.

#### OR

- (b) Discuss charact. Of ideal switch & explain each in detail.
- Q.3 (a) Define commutation. Describe thyrister turn off mechanism in detail. List the 07 method of commutation.
  - (b) What is inverter! Explain classification of inverter in details. List the 07 requirement of practical inverter.

#### OR

- Q.3 (a) Define turn on time. Describe thyrister turn on mechanism in detail. List the 07 method of triggering.
  - (b) Explain classification of chopper. Explain working of step down chopper using 07 circuit diagram &neat waveform.
- Q.4 (a) Define s.m.p.s. Explain the classification of it & also, explain working of 07 s.m.p.s with necessary block diagram.
  - (b) Define u.p.s. Explain the classification of it & also, explain working of u.p.s. 07 with necessary block diagram.

### OR

- Q.4 (a) Compare the following terms: 1.induction & dielectric heating.2.Conventional 07 & load proportional capacity modulated heat pump.
  - (b) Compare the following terms: 1.AC & DC motor drive 2.Electroplating & 07 electroforming.
- Q.5 (a) Explain the working, advantages, disadvantages & application of electronic 07 ballast using block diagram.
  - (b) Explain the configuration of H.V.D.C. transmission along with its 07 advantages, disadvantages & application.

#### OR

- Q.5 (a) Define electrical welding. Explain the working, advantages, disadvantages & 07 application of switched mode arc welder using block diagram.
  - (b) Explain the utilization of non conventional energy sources in power **07** generation using power electronics with necessary diagram.

07

\*\*\*\*\*