Seat No.:	Enrolment No.

Subject Code: 160801

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-VI • EXAMINATION - WINTER • 2014

Date: 26-11-2014

	•	Code: 160801 Date: 26-11-2014	
Tin	•	Name: Integrated Circuits and Application 2:30 pm - 05:00 pm Total Marks: 70	
Histi	1. 2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a)	Draw and Explain the block diagram representation of a typical Op-Amp.	07
	(b)	Draw and explain the functional block diagram of IC 555.	07
Q.2	(a)	What is an ideal Op-Amp? Explain the equivalent circuit of an Op-Amp.	07
	(b)	Explain following performance parameters of Op-Amp. (i) Input Offset Voltage (ii) Input Offset Current (iii) Input Bias Current (iv) CMRR (v) Slew Rate.	07
		OR	
	(b)	Derive the expression for Voltage gain (A_V) and input resistance with feedback (R_{iF}) for voltage series feedback amplifier.	07
Q.3	(a)	Draw non-inverting amplifier using Op-Amp and derive the expression for its output voltage.	07
	(b)	Explain the Peaking Amplifier.	07
		OR	
Q.3	(a)	Explain the Ideal and practical differentiator circuit with its frequency response.	07
	(b)	Explain Instrumentation Amplifier using transducer bridge with its application.	07
Q.4	(a)	Describe a sample and hold circuit and give its applications.	07
	(b)	What are precision rectifiers? Explain the operation of half wave positive & negative precision rectifier. OR	07
Q.4	(a)	Explain the operation of Phase Locked Loop with its block diagram	07
	(b)	Explain IC 555 as a Monostable multivibrator with wave shaping network. Design the circuit to produce a time delay of 10ms.	07
Q.5	(a)	Explain Astable multivibrator using Op-Amp.	07
	(b)	Write short note on Basic Log Amplifier using diode. OR	07
Q.5	(a) (b)	Explain summing, scaling and averaging amplifier using Op-Amp. Write a short note on Schmitt trigger.	07 07
