Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-VI • EXAMINATION - WINTER • 2014

Subject Code: 160905

Date: 03-12-2014

Subject Name: Electrical and Electronic Measurement Time: 02:30 pm - 05:00 pm

Total Marks: 70

07

Instructions:

- 1. Attempt all questions.
- Make suitable assumptions wherever necessarv. 2.
- 3. Figures to the right indicate full marks.
- Q.1 Discuss with suitable examples different types of systematic errors. (a)
 - Explain salient features of Maxwell's Inductance capacitance bridge. Draw phasor 07 **(b)** diagram and derive balance equation.
- Q.2 A four branch bridge network ABCD balanced at 1000 Hz has branches AB and BC 07 (a) of pure resistance of 1000 Ω and 1250 Ω respectively. An unknown impedance forms the arm CD and the branch DA consists of a standard capacitor of 0.1µF capacity and negligible resistance, connected in series with a non inductive resistance of 10Ω to give balance. The supply voltage is 15 V and it is given at points B and D. Determine the components of unknown impedance. Draw necessary phasor diagram. 07
 - **(b)** Draw and explain the Wien bridge.

- Two resistors are specified as $R_1 = 35\Omega \pm 5\%$ and $R_2 = 75\Omega \pm 4\%$. Determine the **(b)** 07 magnitude of limiting error in ohms and in percentage if the two resistances are connected in (a) series and (b) parallel.
- 0.3 Derive the equation of unknown resistance of Kelvin's double bridge under balanced 07 (a) condition.
 - What is the importance of the value of Earth's resistance? What are the factors which 07 **(b)** influence its value? Describe in brief the fall of potential method for measurement of earth resistance.

OR

- A Kelvin's bridge is balanced with following constants: Outer ratio arm 100 Ω and Q.3 07 **(a)** 1000 Ω ; inner arms ratio 99.92 Ω and 1000.6 Ω ; Resistance of link 0.1 Ω ; Standard resistance 0.00377 Ω . Calculate the value of unknown resistance. Write short note on Megger. 07 **(b)** Q.4 Explain comparison method of testing of C.T. 07 (a) Discuss frequency selective wave analyzer. 07 **(b)** OR
- Derive equation for ratio and phase angle error of a P.T. **O.4 (a)** 07 **(b)** Explain heterodyne wave analyzer. 07 Q.5 Discuss Campbell's bridge method to measure iron losses. 07 (a)
 - Explain Varley loop test to determine the location of cable fault. **(b)** 07 OR
- **(a)** 07 Q.5 Explain flux meter with suitable diagram. Discuss the continuity test conducted on long length cables. 07 **(b)** *******