Seat No.: \_\_\_\_\_

Enrolment No.

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER-VII • EXAMINATION - WINTER • 2014** Subject Code:170801 Date: 25-11-2014 **Subject Name: Power Electronics and Industrial Drives Total Marks: 70** Time: 10:30 am - 01:00 pm Instructions: 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. **Q.1** (a) Explain about the construction, characteristics and gate drive requirements of SCR. 07 (b) With neat sketch describe the operation of half wave uncontrolled rectifier with R-07 L load. **Q.2** The three phase full wave rectifier has a load of L=1.5 mHz, R=2.5 $\Omega$  and E=10 V. 07 (a) The input voltage is Vin =208V,60 Hz. Determine 1. The steady state load current Io at  $\omega = \pi/3$ 2. The average diode current Io 3. The rms diode current Ir 4. The rms output current Irms. Explain Turn-off mechanism in Thyristor. Explain commutation methods of 07 **(b)** Thyristors briefly. OR **(b)** What is VSI? Describe the operation of single phase half bridge VSI. Also state the 07 switching state table for the same. **Q.3** (a) Explain the following PWM methods for control of single phase inverter 07 • Single pulse width modulation. • Sinusoidal pulse width modulation. (b) Briefly discuss the 120 degree operation of inverter circuit with appropriate 07 waveforms. OR Discuss the class B operation of Chopper Circuit. Q.3 07 (a) What is DC drive? Discuss basic characteristics of DC motors. **(b)** 07 (a) Discuss the role of snubber circuit from protection aspect. 07 0.4 A single phase half wave AC voltage controller has a resistive load of 10 + and the 07 **(b)** input voltage is 120 V, 60 Hz. The delay angle of thyristor is 90°. Determine (a) RMS value of the output voltage (b) the input Power Factor (c) the average input current. OR (a) Discuss about choice of AC and DC drive in detail. 07 **O.4** (b) Discuss operation of 3-phase ac to ac converter with star connected resistive load. 07 Briefly discuss the operation of current source inverter with necessary waveform. 07 0.5 (a) (b) Briefly discuss the operation of single phase semi converter d.c. drives. 07 OR (a) Explain three phase cycloconverter and sinusoidal harmonic reduction techniques for 07 Q.5 cycloconverter. (b) Classify synchronous motor drives. Explain brushless DC and AC motor. 07

\*\*\*\*\*