	GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-III • EXAMINATION – WINTER • 2014		
	Subject Code: 2131006 Date: 18-12-2014		
	Subject Name: Electronics Devices and Circuits		
		ne: 02.30 pm - 05.00 pm Total Marks: 70	
	Inst	ructions:	
		<ol> <li>Attempt all questions.</li> <li>Make suitable assumptions wherever necessary.</li> </ol>	
		3. Figures to the right indicate full marks.	
Λ1	(a)	Define the fellowing towns	07
Q.1	(a)	Define the following terms: (1) Doping (2) Clipper (3) Diffusion (4) Static Resistance	U/
		(5) Drift current (6) Bulk Resistance (7) Barrier Potential	
	<b>(b)</b>	Give the comparison between half wave rectifier, full wave rectifier and bridge	07
		rectifier with the help of following points:  a) No of diodes  b) Transformer necessity  c) PIV ratings	
		d) Average dc current e) Average dc voltage f) rms current	
		g) Ripple factor h) Rectifier efficiency	
Q.2	(a)	Draw and explain the input and output characteristics of common emitter	07
	\	configuration.	
	<b>(b)</b>	What is voltage multiplier? Draw and explain full wave voltage doubler.  OR	07
	<b>(b)</b>	Describe the construction, the symbol, V-I characteristics and application of	07
		varactor diode.	
Q.3	(a)	What is multistage amplifier? Explain in detail with neat diagram two stages RC	07
		coupled amplifier.	
	<b>(b)</b>	What is the need of biasing the transistor? Describe the voltage divider bias circuit.  OR	07
Q.3	(a)	What is voltage regulation? Explain the working of two transistor regulator.	07
	<b>(b)</b>	Design a fixed bias circuit biased using NPN transistor which has $\beta$ =150.The dc	<b>07</b>
		biasing point at $V_{CE}=5V$ and $I_{C}=5mA$ . Supply voltage ( $V_{CC}$ ) is 10V.	
<b>Q.4</b>	(a)		<b>07</b>
	<b>(b)</b>	with negative feedback with the use of block diagram.  Compare :(1) BJT with FET (2) Small signal amplifier and large signal amplifier	07
	(D)	OR	U/
Q.4	(a)	Derive input resistance for voltage shunt feedback amplifier and current series	<b>07</b>
	(b)	feedback amplifiers based on position of O point. Show the officiency of class A	07
	<b>(b)</b>	Classify amplifiers based on position of Q-point. Show the efficiency of class-A transformer coupled amplifier is 50%.	07
0.5	(a)	Draw and explain the construction, operation and drain characteristic of	07
Q.5	(a)	N-channel JFET.	U/
	<b>(b)</b>	Explain the working of emitter follower. Draw the ac equivalent circuit and	<b>07</b>
		determine the AC emitter resistance, voltage gain and input impedance.	
		OR	
Q.5	(a)	An amplifier gain changes by $\pm 10\%$ without any feedback. Using negative	07
		feedback the amplifier is to be modified to yield a gain of 100 with $\pm 0.1\%$	
		variation. Find the required open loop gain of the amplifier and the amount of negative feedback.	
	<b>(b)</b>	What is MOSFET? Compare depletion type and enhancement type MOSFET.	07

\*\*\*\*\*\*

Enrolment No.\_\_

Seat No.: \_\_\_\_