

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Semester -IV Remedial Examination December - 2010****Subject code: 341102****Subject Name: Electronics Instrument & Measurements****Date: 16 /12 /2010****Time: 02.30 pm – 05.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is Authentic

- Q.1** (a) Explain the following terms related to measuring instruments **04**
 1) Accuracy 2) Sensitivity 3) Resolution 4) Precision
- (b) List the various sources of possible errors in instruments, explain limiting error. **03**
- (c) With circuit diagram describe the working of the Whestone bridge. Derive Null condition equation and give its application. **07**
- Q.2** (a) Describe Wein's bridge. Obtain equation to find frequency and give application of Wein's bridge. **07**
- (b) Explain working of Kelvin's double arm bridge and derive an expression for finding unknown resistance. **07**
- OR**
- (b) Derive the equation for moving iron type instrument and compare it with moving coil instrument. **07**
- Q.3** (a) With block diagram describe Q meter. Give the Application and source of errors of a Q meter. **07**
- (b) Explain ramp type DVM with neat sketch. Give application of digital voltmeter. **07**
- OR**
- Q.3** (a) With block diagram describe construction and working of CRO. Give application of CRO **07**
- (b) What is the importance of Delay line in vertical deflection system of CRO. Give the advantages of digital storage oscilloscope. **07**
- Q.4** (a) With the help of block diagram explain **07**
 i) Function generator ii) Sweep frequency generator
- (b) With circuit diagram describe working of astable multivibrator, draw necessary waveforms. **07**
- OR**
- Q. 4** (a) Explain with block diagram working of digital frequency counter. **07**
- (b) Explain in detail different types of measurement errors of frequency counter. **07**
- Q.5** (a) Give classification of transducers. Define "Gauge factor" of strain gauge. Obtain the expression for gauge factor in terms of Poisson's ratio **07**
- (b) Explain construction and application of thermocouple and piezoelectric transducers **07**
- OR**
- Q.5** (a) Write short note : i) Digital IC tester ii) Logic Analyzer **07**
- (b) Explain construction, working principle and application of LVDT **07**

| | | | |
|----------|---|---|----|
| પ્રશ્ન-૧ | અ | માપન સાધનના અનુસન્ધાનમા નિચેની વ્યાખ્યા જણાવો. 1)એક્યુરસી 2) સેંસીટીવિટી 3) રીઝોલ્યુશન 4) પ્રીસીશન | 04 |
| | બ | માપન સાધન ની ક્ષતિઓ ની યાદી આપો. લિમિટિંગ ક્ષતિ ને સમજાવો. | 03 |
| | ક | પરીપથ દોરી વ્હીસ્ટન બ્રિજ ની કાર્ય પદ્ધતી સમજાવો.નલ કંડિશન માટે નું સુત્ર જણાવો અને તેની ઉપયોગીતાઓ જણાવો. | 07 |
| પ્રશ્ન-૨ | અ | વીન્સ બ્રિજ જણાવો. આવૃત્તિ માટે નું સુત્ર શોધો અને વીન્સ બ્રિજ ની ઉપયોગીતા જણાવો. | 07 |
| | બ | કેલવિન ડબલ આર્મ બ્રિજ ની કાર્ય પદ્ધતી સમજાવો અને અજાણ અવરોધ શોધવાનું સુત્ર શોધો. | 07 |
| | | અથવા | |
| | બ | મુવીંગ આયર્ન પ્રકારના સધન નું સુત્ર જણાવો અને તેની તુલના મુવીંગ કોઇલ માપન સાથે કરો. | 07 |
| પ્રશ્ન-૩ | અ | ખંડીય આકૃતિ દોરી ‘ક્યુ’ મીટર સમજાવો.તેની ઉપયોગીતા આપો અને ‘ક્યુ’ મીટર માં ઉદ્ભવતી ક્ષતિઓ જણાવો. | 07 |
| | બ | રેમ્પ પ્રકારના ડી.વી.મ ની આકૃતિ દોરી સમજાવો અને ડી.વી.મ ની ઉપયોગીતા જણાવો. | 07 |
| | | અથવા | |
| પ્રશ્ન-૩ | અ | કેથોડ રે ઓસિલોસ્કોપ ની ખંડીય આકૃતિ દોરી કાર્ય પદ્ધતી સમજાવો. | 07 |
| | બ | કેથોડ રે ઓસિલોસ્કોપ માં વર્ટીકલ ડીફ્લેક્શન શું છે તેની અગત્યતા સમજાવો. સ્ટોરેજ ઓસિલોસ્કોપ ના ફાયદા જણાવો. | 07 |
| પ્રશ્ન-૪ | અ | ખંડીય આકૃતિ દ્વારા સમજાવો ૧)ફ્લેક્શન જનરેટર ૨) સ્વીપ ફ્રિક્વેન્સી જનરેટર | 07 |
| | બ | પરીપથ દોરી એસ્ટેબલ મલ્ટીવાઇબ્રેટરની કાર્ય પદ્ધતી સમજાવો અને યોગ્ય તરંગો દોરો. | 07 |
| | | અથવા | |
| પ્રશ્ન-૪ | અ | ખંડીય આકૃતિ દ્વારા ડિજિટલ ફ્રિક્વેન્સી કાઉંટર સમજાવો. | 07 |
| | બ | ફ્રિક્વેન્સી કાઉંટરની અલગ અલગ પ્રકારની ક્ષતિઓ વિસ્તારપૂર્વક સમજાવો. | |
| પ્રશ્ન-૫ | અ | ટ્રાંસડ્યુસરનું વર્ગીકરણ કરો. સ્ટ્રેન્જોજના ગેજ ફેક્ટરની વ્યાખ્યા લખો. પોઇઝન રેશિયોના સંદર્ભમા ગેજ ફેક્ટરનું સુત્ર તારવો. | 07 |
| | બ | થર્મોકપલ અને પિઝોઇલેક્ટ્રિક ટ્રાંસડ્યુસરની બનાવટ અને ઉપયોગીતા સમજાવો. | 07 |
| | | અથવા | |
| પ્રશ્ન-૫ | અ | ટુંક નોંધ લખો: ૧)ડિજિટલ આયસી ટેસ્ટર ૨)લોજિક એનેલાયઝર | 07 |
| | બ | એલ.વી.ડી.ટી ની બનાવટ, કાર્ય પદ્ધતી અને ઉપયોગીતા સમજાવો. | 07 |
