

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY
Diploma Engineering - SEMESTER-VI • EXAMINATION – SUMMER 2013

Subject Code: 360906

Date: 17/05/2013

Subject Name: Power Electronics

Time: 10:30 am TO 01:00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

Q.1	(a) Draw Symbol, Construction & Working principle of (1) DIAC (2) IGBT	07
	(b) Explain UJT relaxation oscillator.	07
Q.2	(a) What is commutation in S.C.R.? Explain any two commutation method in S.C.R.	07
	(b) Draw Snubber circuit and explain its working.	07
	OR	
	(b) Explain ratings of the S.C.R.	07
Q.3	(a) What is a Chopper? Explain different methods for obtaining voltage control in chopper circuit.	07
	(b) Explain the basic principle of Inverter circuit. Explain Parallel Inverter circuit.	07
	OR	
Q.3	(a) Draw and explain John's Chopper circuit.	07
	(b) Draw & Explain the block diagram of UPS.	07
Q.4	(a) Explain basic principle of Cycloconverter. What are the different types of Cycloconverters?	07
	(b) Draw & Explain speed control of D.C motor by means of PLL control.	07
	OR	
Q. 4	(a) Write down the Advantages, Disadvantages & applications of Cycloconverter.	07
	(b) Explain speed control of universal motor using SCR.	07
Q.5	(a) Draw& Explain block diagram of Robotics Systems.	07
	(b) Short note on G.T.O.	07
	OR	
Q.5	(a) State different applications of Robots.	07
	(b) Short note on LASCR.	07

પ્રશ્ન-૧	અ	નીચેનાની સંજ્ઞા, રચના અને કાયોસિક્ષાંત લખો. (1) ડાયક (2) આઈજીબીટી	07
	બ	UJT રીલેક્શેસન ઓસીલેટર સમજાવો.	07
પ્રશ્ન-૨	અ	S.C.R. માં કોમ્યુટેશન શું છે? S.C.R. માટે ગમે તે બે કોમ્યુટેશનની રીત વર્ણાવો.	07
	બ	સન્બર પરીપથ દોરો અને તેનું કાર્ય વર્ણાવો. અથવા	07
	બ	S.C.R.નું રેટીંગ વર્ણાવો.	07
પ્રશ્ન-૩	અ	ચોપર એટલે શું? ચોપર પરિપથમા વોલ્ટેજ કંન્ટ્રોલ મેળવવા માટેની વિવધ પદ્ધતિઓ લખો અને સમજાવો.	07
	બ	ઇન્વર્ટર પરિપથનો પાયા નો સિદ્ધાંત સમજાવો. સમાંતર ઇન્વર્ટર પરિપથ સમજાવો. અથવા	07
પ્રશ્ન-૩	અ	જોકની ચોપર સરકીટ દોરી સમજાવો.	07
	બ	U.P.S. ની ખંડ આફ્ટ્ટી દોરી સમજાવો.	07
પ્રશ્ન-૪	અ	સાયક્લોકન્વર્ટરનો બેઝીક સિદ્ધાંત સમજાવો. સાયક્લોકન્વર્ટરના અલગા અલગ પ્રકારો કયા છે?	07
	બ	ડીસી. મોટર નો સ્પીડ કન્ટ્રોલ પી.એલ.એલ કન્ટ્રોલની મદદથી દોરીને સમજાવો. અથવા	07
પ્રશ્ન-૪	અ	સાયક્લોકન્વર્ટરના ફાયદાઓ, ગેરફાયદાઓ અને તેના ઉપયોગો લખો	07
	બ	યુનિવર્સલ મોટર નો SCR ની મદદ થી થતો સ્પીડ કન્ટ્રોલ સમજાવો.	07
પ્રશ્ન-૫	અ	ખંડ આફ્ટ્ટીની મદદથી રોબોટિક્સ સીસ્ટમ દોરો અને સમજાવો.	07
	બ	G.T.O. વિષે ટ્રકનોંધ લખો.	07
પ્રશ્ન-૫	અ	રોબોટના અલગ અલગ ઉપયોગો લખો.	07
	બ	LASCR વિષે ટ્રકનોંધ લખો.	07
