

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-I • EXAMINATION – SUMMER • 2014****Subject Code: 3310702****Date: 21-06-2014****Subject Name: Fundamentals of Digital Electronics****Time: 02:30 pm- 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make Suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Use of programmable & Communication aids are strictly prohibited.
5. Use of only simple calculator is permitted in Mathematics.
6. English version is authentic.

- Q.1** Answer any seven out of ten. **14**
1. Convert $(100.50)_{10}$ into Octal and Hexadecimal.
 2. Convert $(AF)_{16}$ into decimal number system.
 3. Briefly explain Excess-3 code.
 4. What is difference between BCD and Binary number system?
 5. Draw truth table of following gates.
(I) NAND (II) EX-OR
 6. What is difference between encoder and decoder?
 7. Perform binary additions: $(11011011)_2 + (01011101)_2$
 8. Draw symbols of following gates
(I) NOR (II) Bubbled OR gate
 9. Simplify : $A(A' + C) (A'B + C')$
 10. Define: Don't Care variable, I.C., MSB
- Q.2** (a) With suitable example explain canonical or standard forms **04**
OR
- (a) Explain 1's complement and 2's complement with suitable example. Show the subtraction using complements. **04**
- (b) Simplify and draw digital circuit for following equation. $F = \sum m(0,2,6,10,11,12,13)$ Don't care $d(3,4,5,14,15)$ **05**
OR
- (b) Simplified POS expression using K-Map method for $F(A,B,C,D) = \prod m(0, 1, 5, 8, 9, 10)$ and implement using NOR logic **05**
- (c) Write short note: D'Morgan's laws. **05**
OR
- (c) Draw the logic circuit using NOR gates for the Boolean expression $A = XY' + X'Y + Z$ **05**
- Q.3** (a) Briefly explain Universal Gates. Design OR gate using NAND gate. **05**
OR
- (a) Subtract $(100010)_2$ from $(1000000)_2$ using 2's complement method. **05**
- (b) Draw truth table for full adder circuit and write equation for sum of three inputs. **05**
OR
- (b) What is difference between half subtractor and full subtractor ? Explain half subtractor. **05**
- (c) What do u mean by logic gate? Draw symbol and prepare truth table for NOT, OR, AND. **04**

OR

(c)	Discuss need of simplification of Boolean equation in digital system.	04
Q.4	(a) Draw and explain 4-bit parallel adder.	04
	OR	
(a)	What is difference between decoder and multiplexer?	04
(b)	Design logic circuit for 3 to 8 decoder.	04
	OR	
(b)	Write short note: 4 x 1 Multiplexer.	04
(c)	What do u mean by Integrated circuit? Explain MSI IC and discuss any one MSI combinational design.	06
Q.5	(a) Design an excess-3-to-BCD code converter.	07
	(b) Draw logic circuit for 4- 2 encoder.	04
	(c) What is difference between SSI and MSI IC?	03

ગુજરાતી

પ્રશ્ન. ૧	દશમાંથી કોઈપણ સાતના જવાબ આપો.	૧
		૪
૧.	$(100.50)_{10}$ ને ઓક્ટેલ અને હેક્ઝાડેસીમલ માં રૂપાંતરિત કરો.	
૨.	$(AF)_{16}$ ને દશાંશ પદ્ધતિ માં રૂપાંતર કરો.	
૩.	Excess-3 કોડ ને ટ્રૂકમાં સમજાવો.	
૪.	BCD અને Binary નંબર પદ્ધતી વચ્ચે શું તફાવત છે ?	
૫.	નીચેના ગેટના truth table દોરો. (I) NAND (II) EX-OR	
૬.	encoder અને decoder વચ્ચે શું તફાવત છે?	
૭.	Binary સરવાળો કરો : $(11011011)_2 + (01011101)_2$	
૮.	નીચેના ગેટના સંકેત દોરો. (I) NOR (II) Bubbled OR gate	
૯.	સરલીકરણ : $A(A' + C)(A'B + C')$	
૧૦	ટુકમાં સમજાવો :- Don't Care variable, I.C., MSB	
પ્રશ્ન -૨	અ યોગ્ય ઉદાહરણ સાથે canonical or standard forms સમજાવો.	૦૪
	અથવા	
અ	1's complement અને 2's complement ઉદાહરણ સાથે સમજાવો. Subtraction ને complements નો ઉપયોગ કરી સમજાવો.	૦૪
બ	K-Map નો ઉપયોગ કરી આપેલા સમીકરણનો સરળીકરણ કરો. $F = \sum_m(0,2,6,10,11,12,13)$ ડોન્ટ કેર $d(3,4,5,14,15)$	૦૫
	અથવા	
બ	K-Map નો ઉપયોગ કરી POS સમીકરણથી $F(A,B,C,D) = \prod_m(0, 1, 5, 8, 9, 10)$ સરલીકરણ કરો અને NOR logic થી રચના કરો.	૦૫
ક	ટુકનોંધ લાખો : D'Morgan's laws.	૦૫

OR

- ક NOR ગેટ ની મદદથી નીચેની Boolean સમીકરણની લોજિક સર્કિટ દોરો. 0૫
 $A = XY' + X'Y + Z$
- પ્રશ્ન -૩ અ Universal Gates શું છે? NAND ની મદદથી OR gate મેળવો. 0૫
અથવા
- અ $(100010)_2$ ને $(1000000)_2$ 2's complement ની મદદથી બાદબાકી કરો. 0૫
બ Full adder સર્કિટ માટે truth table લખો અને ત્રણ ઇનપુટ ના સમીકરણનો સરવાળો લખો. 0૫
અથવા
- બ Half subtractor અને full subtractor વચ્ચે શું તફાવત છે? half subtractor સમજાવો. 0૫
ક Logic gate વિષે તમારો શું મંતવ્ય છે ? NOT, OR, AND gate માટે સંકેત દોરો અને truth table લખો. 0૪
અથવા
- ક Digital પ્રણાલીમાં Boolean સમીકરણ ના સરલીકરણ ની જરૂરિયાત જાણવો. 0૪
- પ્રશ્ન -૪ અ 4-bit parallel adder દોરો અને સમજાવો. 0૪
અથવા
- અ Decoder અને multiplexer વચ્ચે શું તફાવત છે? 0૪
બ 3 to 8 decoder ની logic સર્કિટ દોરો. 0૪
અથવા
- બ ટુકનોંધ લાખો: 4 x 1 Multiplexer. 0૪
ક Integrated circuit વિષે તમારો શું મંતવ્ય છે? MSI IC સમજાવો અને કોઈપણ એક MSI combinational રચના સમજાવો. 0૬
- પ્રશ્ન -૫ અ Excess-3-to-BCD code converter ની રચના સમજાવો . 0૭
બ 4- 2 encoder ની logic સર્કિટ દોરો. 0૪
ક SSI and MSI IC વચ્ચે શું તફાવત છે? 0૩
