

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-III • EXAMINATION – SUMMER • 2014****Subject Code: 331102****Date: 25-06-2014****Subject Name: Digital Electronics****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Each question carry equal marks (14 marks)

- Q.1** (a) Convert the decimal number 1024 into Binary, Octal and Hexadecimal numbers. **07**
- (b) Perform following binary arithmetic operations: **07**
 (i) $101111 + 111010$ (ii) $1100 - 1011$ (iii) 1011×110
 (iv) $101010 \div 100$
- Q.2** (a) Write the name of basic logic gates and explain them using their truth table. **07**
- (b) Write the name of various logic families and make comparison between them. **07**
- OR
- (b) Explain the Karnaugh map method of simplification of Boolean equation using suitable example. **07**
- Q.3** (a) Write the name of universal gates. Prove any one as universal gate. **07**
- (b) Explain various laws and theorems of Boolean algebra. **07**
- OR
- Q.3** (a) (i) Compare static and dynamic RAM. (ii) Explain ROM, PROM, EPROM **07**
- (b) Explain about the specifications of D to A converter. **07**
- Q.4** (a) What is full adder? Draw its logic circuit and explain it with its truth table. **07**
- (b) Write short note on: 4-bit binary parallel adder. **07**
- OR
- Q.4** (a) Simplify following Boolean expressions: **07**
 (i) $Y = A'BC + ABC + BC'$ (ii) $Y = AB'C + ABC + A'C$
- (b) Write the name of different types of Analogue to Digital converters and explain any one method in detail. **07**
- Q.5** (a) Explain about D flip-flop and T flip-flop. **07**
- (b) Draw the logic diagram of 4-bit Serial Input Shift right Register and explain its working with its waveforms. **07**
- OR
- Q.5** (a) Explain Multiplexer circuit with appropriate example and write down its applications. **07**
- (b) Draw the logic circuit of J-K flip-flop and master-slave J-K flip-flop and explain them using their truth tables. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ ડેસિમલ નંબર 1024 ને બાયનરી, ઓક્ટલ અને હેક્સાડેસિમલ નંબરો માં ફેરવો. ૦૭
 બ નીચેના બાયનરી ઓપરેશનો કરો: ૦૭
 (i) $101111 + 111010$ (ii) $1100 - 1011$ (iii) 1011×110
 (iv) $101010 \div 100$
- પ્રશ્ન. ૨ અ બેઝીક લોજીક ગેટના નામ લખો અને તેમને ટ્રુથ ટેબલના ઉપયોગ થી ૦૭
 સમજાવો.
 બ લોજીક ફેમિલિ ના નામ લખો અને તેમની વચ્ચે સરખામણી કરો. ૦૭
 અથવા
 બ બુલિયન સમિકરણ ને સરળ બનાવવા માટે ની Karnaugh મેપ પદ્ધતિ વિશે ૦૭
 યોગ્ય ઉદાહરણ ની મદદથી સમજાવો.
- પ્રશ્ન. ૩ અ યુનિવર્સલ ગેટના નામ લખો. કોઈ પણ એક ગેટને યુનિવર્સલ ગેટ તરીકે સાબિત ૦૭
 કરો.
 બ બુલિયન અલજીબ્રાના નિયમો તથા શિયરમ વિશે સમજાવો. ૦૭
 અથવા
- પ્રશ્ન. ૩ અ (i) સ્ટેટીક અને ડાયનેમિક RAM ની સરખામણી કરો ૦૭
 (ii) ROM, PROM, EPROM સમજાવો.
 બ D to A કન્વર્ટર ના સ્પેશિફિકેશન વિશે સમજાવો. ૦૭
- પ્રશ્ન. ૪ અ કુલ એડર એટલે શું? કુલ એડર ની લોજીક સર્કિટ દોરો અને તેને ટ્રુથ ટેબલ ૦૭
 સાથે સમજાવો.
 બ ટુંક નોંધ લખો : 4-બીટ બાયનરી પેરેલલ એડર ૦૭
 અથવા
- પ્રશ્ન. ૪ અ નીચેના બુલિયન એક્સ્પ્રેશન ને સરળ બનાવો. ૦૭
 (i) $Y = A'BC + ABC + BC'$ (ii) $Y = AB'C + ABC + A'C$
 બ અલગ અલગ પ્રકારના ડીજીટલ ટુ એનાલોગ કન્વર્ટર ના નામ લખો અને કોઈ ૦૭
 પણ એક પદ્ધતિ વિશે સમજાવો.
- પ્રશ્ન. ૫ અ D flip-flop અને T flip-flop વિશે સમજાવો. ૦૭
 બ 4-બિટ સિરિયલ ઇનપુટ શિફ્ટ રાઇટ રજિસ્ટર નો લોજીક ડાયાગ્રામ દોરો અને ૦૭
 તેનું કાર્ય વેવફોર્મ સાથે સમજાવો.
- અથવા
- પ્રશ્ન. ૫ અ Multiplexer સર્કિટ યોગ્ય ઉદાહરણ સાથે સમજાવો અને તેના ઉપયોગો લખો. ૦૭
 બ J-K flip-flop અને master-slave J-K flip-flop ની લોજીક સર્કિટ દોરો અને ટ્રુથ ૦૭
 ટેબલની મદદ થી સમજાવો.
